


# **Computer Architecture EECS 361**

## **Lecture 7**

### **ALU Design: Division Designing a Single Cycle Datapath**
 
# Review: Unsigned shift-add multiplier (version 1)


- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

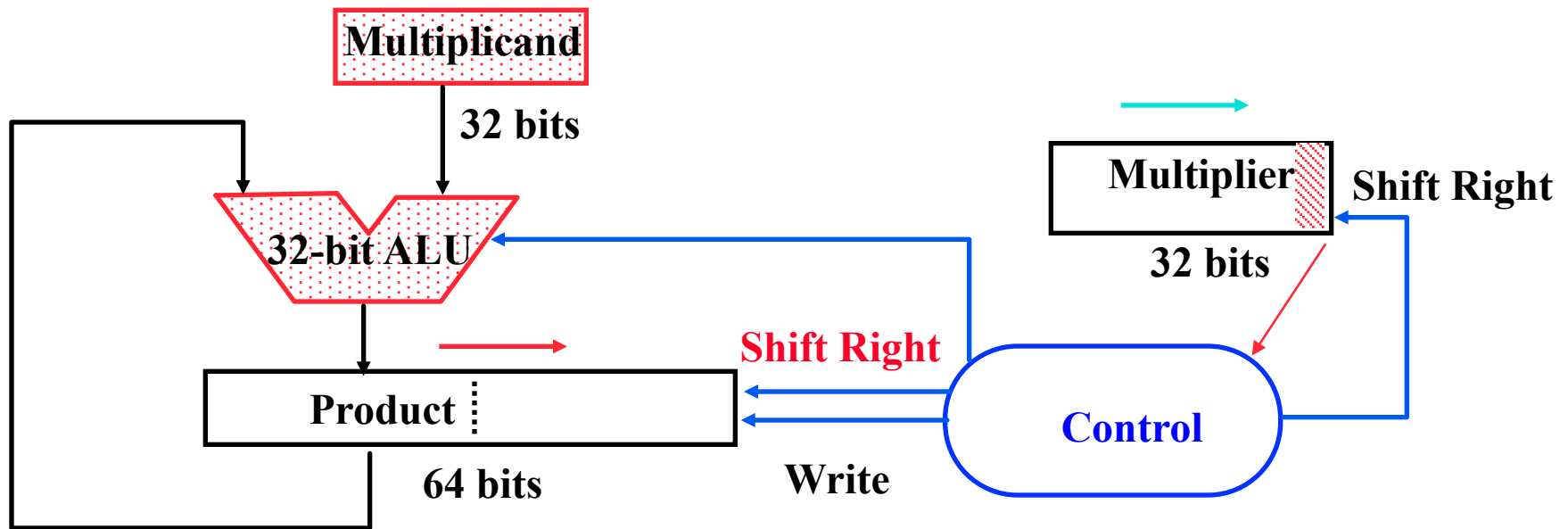
## Review: Unsigned shift-add multiplier (version 2)

- **32-bit** Multiplicand reg, **32-bit** ALU, 64-bit Product reg, 32-bit Multiplier reg



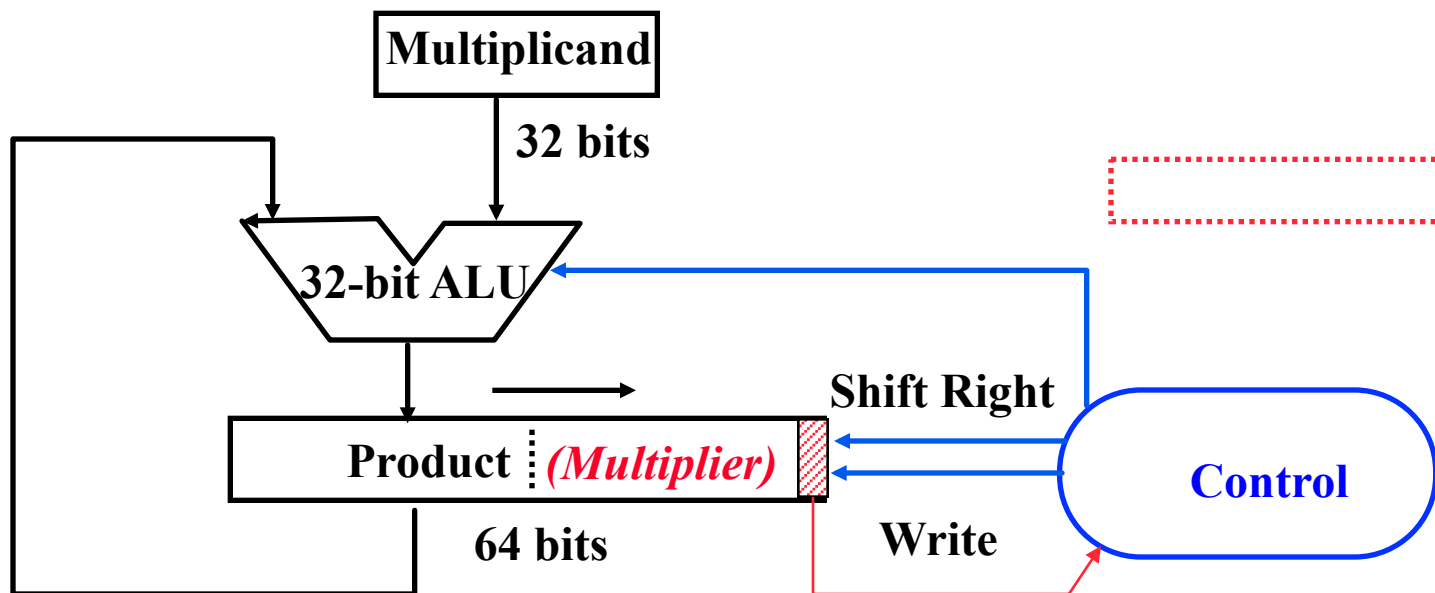
## Review: Unsigned shift-add multiplier (version 3)

- ° 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



# Review: Booth's Algorithm

 

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	00011 <u>11</u> 000
0	1	End of a run of 1s	00 <u>01</u> 111000
0	0	Middle of a run of 0s	0 <u>00</u> 1111000


Originally for Speed since shift faster than add for his machine

$$2^n - 2^k = 00000111111111100000$$


n ..... k ..... 0 (bit position)

# Review: Combinational Shifter from MUXes

Basic Building Block

 

8-bit right shifter

 

- What comes in the MSBs?
- How many levels for 32-bit shifter?
- What if we use 4-1 Muxes ?

# Outline of Today's Lecture

- **Divide**
- **Introduction to Single cycle processor design**

# Divide: Paper & Pencil

		1001	Quotient
Divisor	1000	1001010	Dividend
		<u>-1000</u>	
		10	
		101	
		1010	
		<u>-1000</u>	
		10	Remainder (or Modulo result)

See how big a number can be subtracted, creating quotient bit on each step

Binary => 1 \* divisor or 0 \* divisor

Dividend = Quotient x Divisor + Remainder


=> | Dividend | = | Quotient | + | Divisor |

3 versions of divide, successive refinement


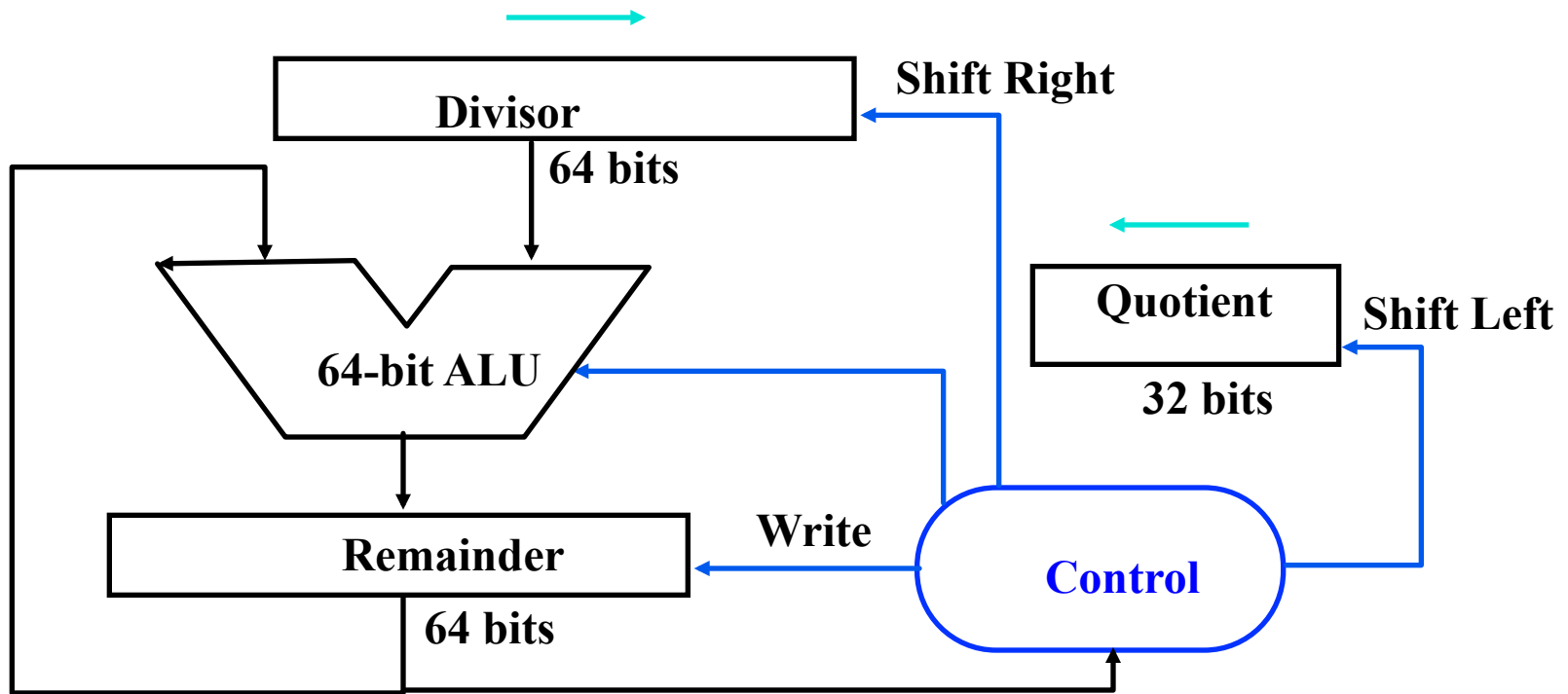
# DIVIDE HARDWARE Version 1


- 64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 1

°Takes  $n+1$  steps for  $n$ -bit Quotient & Rem.

Remainder	Quotient	Divisor
0000	0111	0010
0000		0000

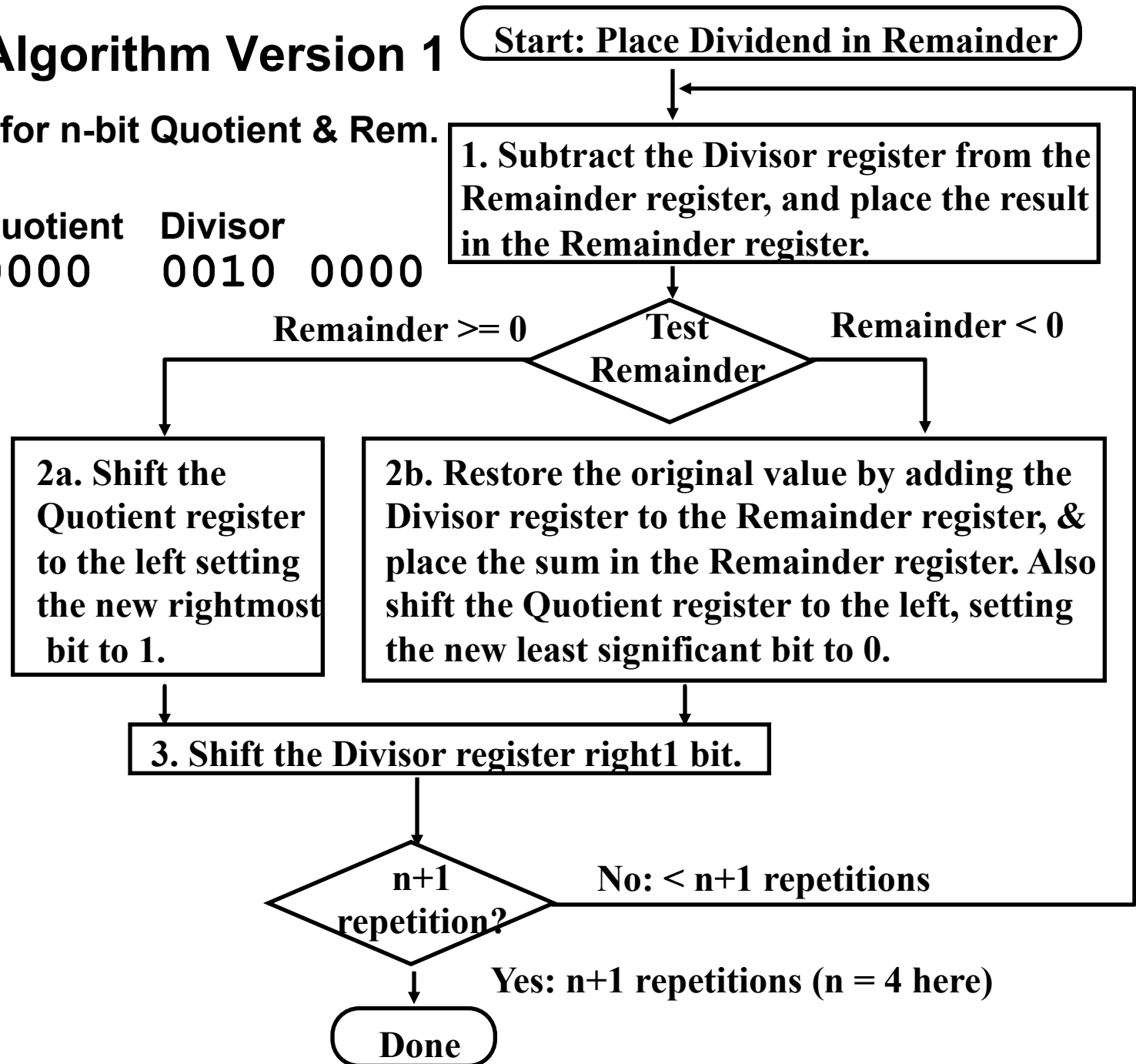


# Observations on Divide Version 1

- **1/2 bits in divisor always 0**  
**=> 1/2 of 64-bit adder is wasted**  
**=> 1/2 of divisor is wasted**
- **Instead of shifting divisor to right,  
shift remainder to left?**
- **1st step cannot produce a 1 in quotient bit  
(otherwise too big)**  
**=> switch order to shift first and then subtract,  
can save 1 iteration**

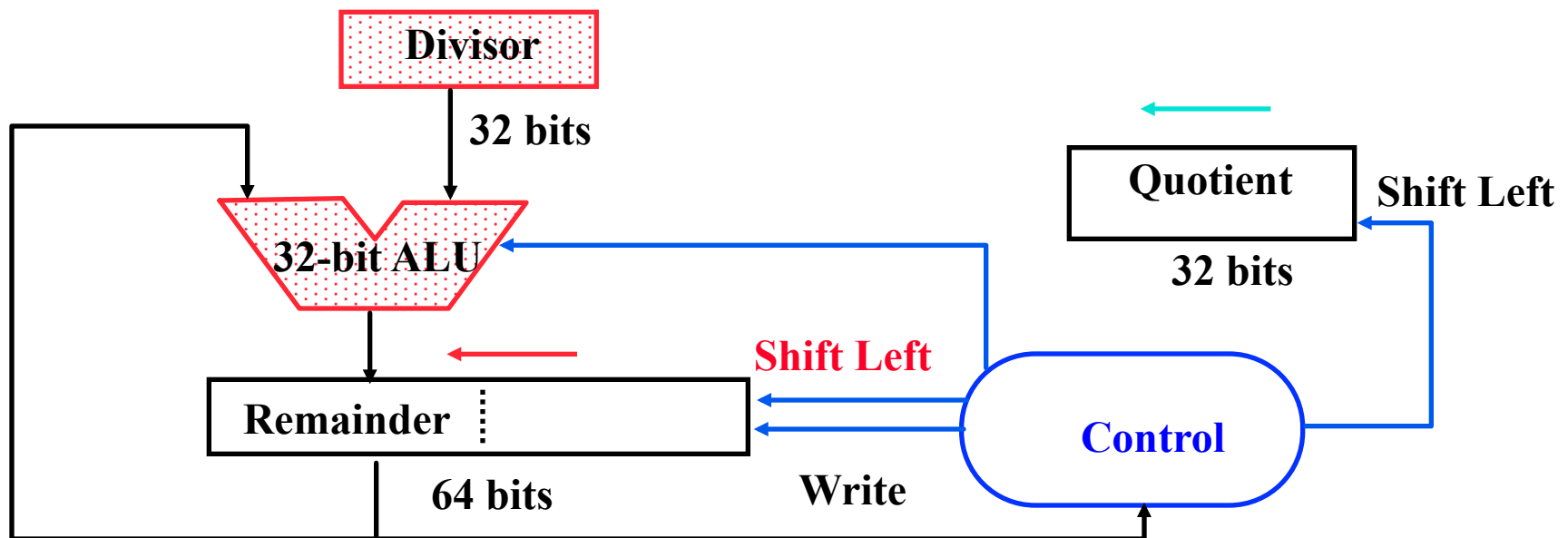
## DIVIDE HARDWARE Version 2

- **32-bit** Divisor reg, **32-bit** ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 2

Remainder	Quotient	Divisor
0000	0111	0000
		0010

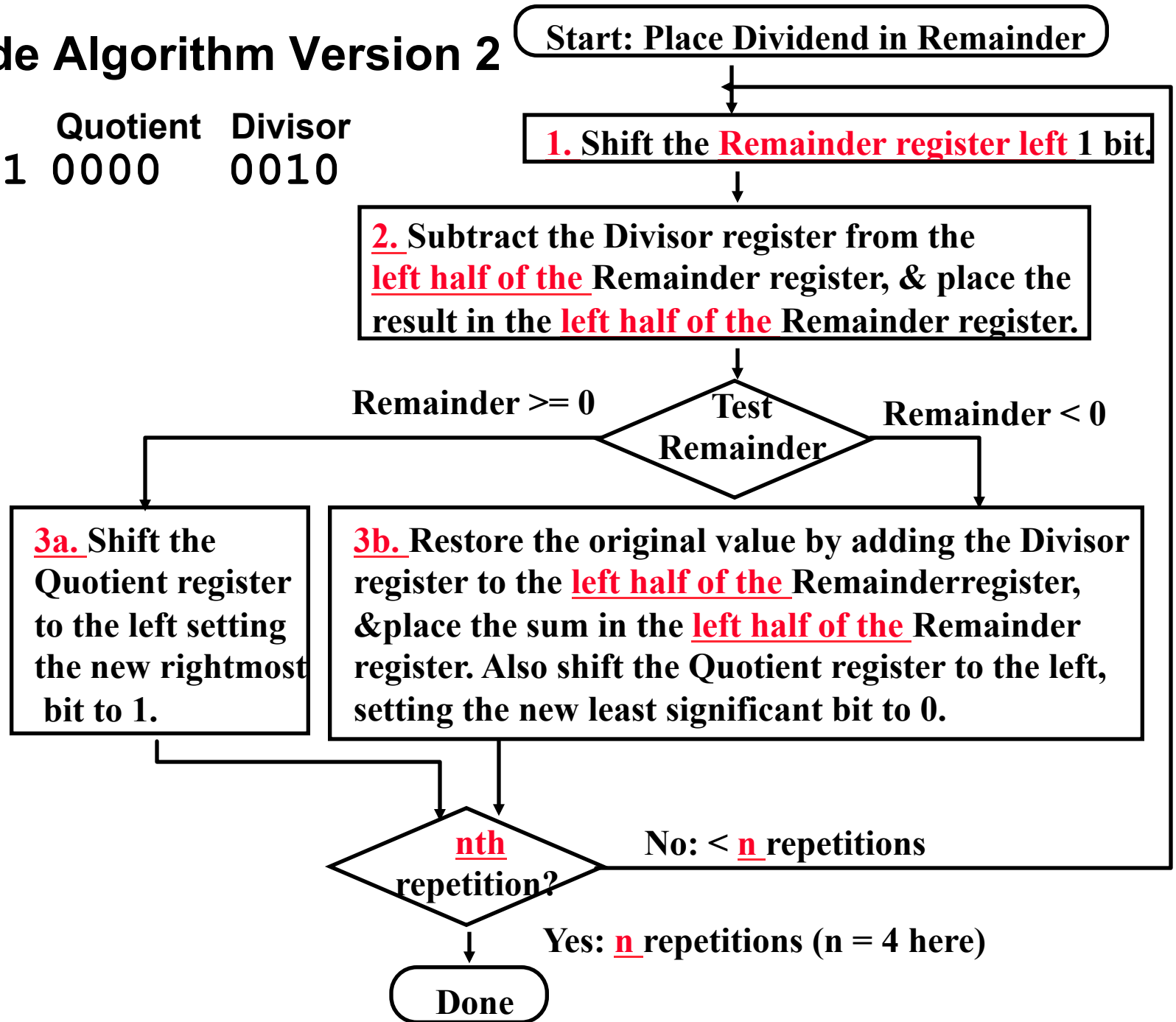


## Observations on Divide Version 2

- **Eliminate Quotient register by combining with Remainder as shifted left**
  - **Start by shifting the Remainder left as before.**
  - **Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half**
  - **The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will be shifted left one time too many.**
  - **Thus the final correction step must shift back only the remainder in the left half of the register**

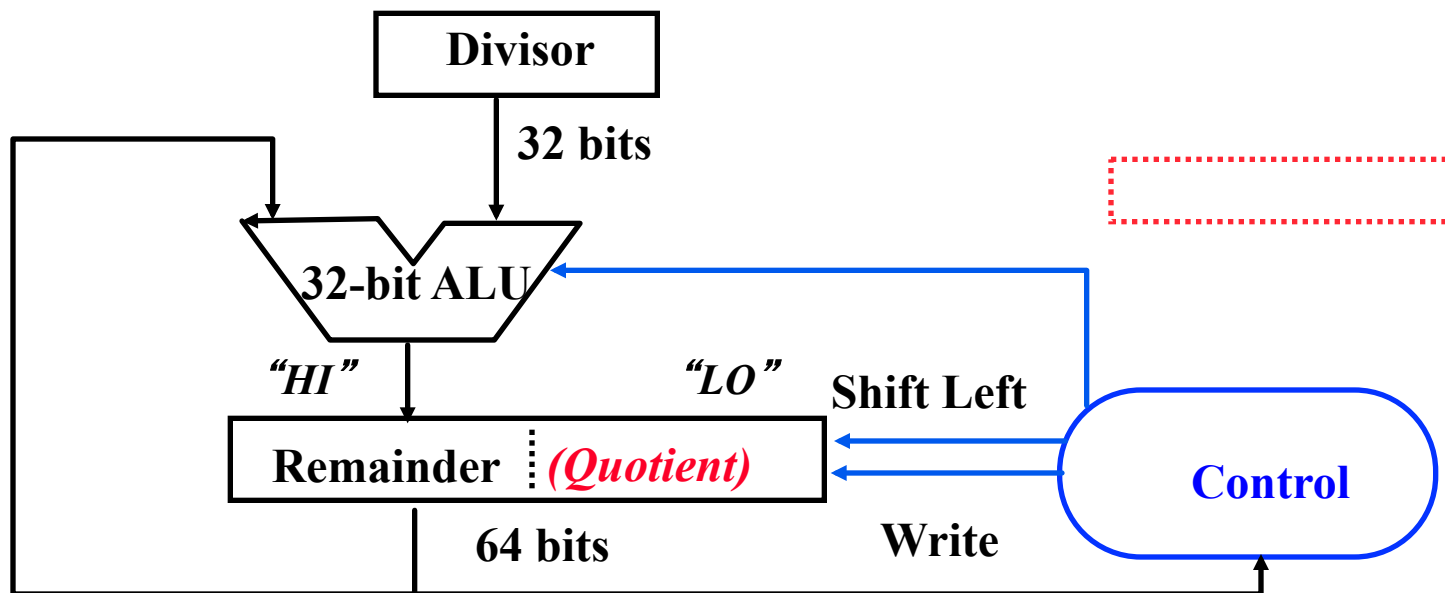
## DIVIDE HARDWARE Version 3

- 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, (0-bit Quotient reg)


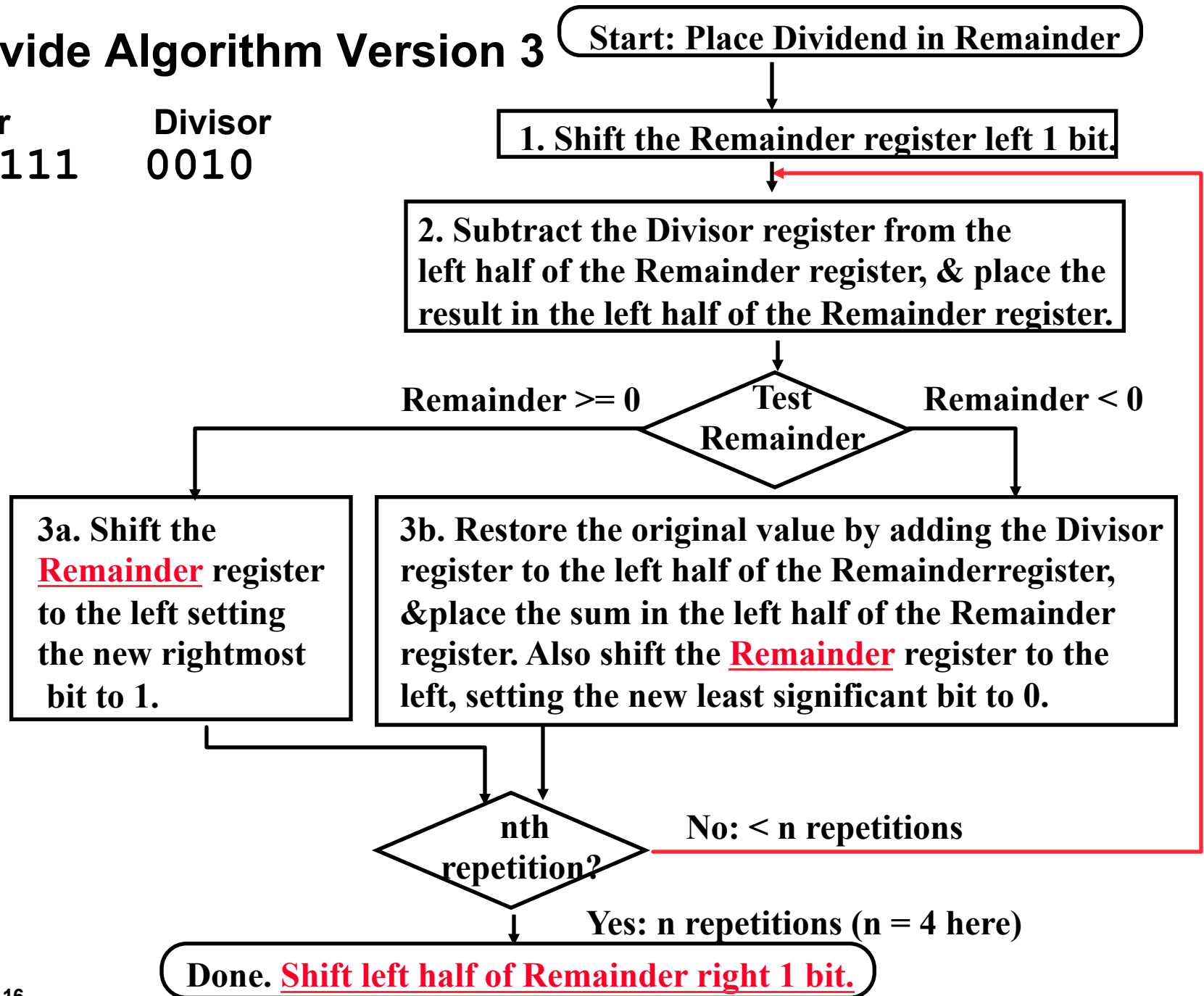
# Divide Algorithm Version 3

Remainder      Divisor  
0000 0111      0010





# Observations on Divide Version 3

- **Same Hardware as Multiply:** just need ALU to add or subtract, and 63-bit register to shift left or shift right
- **Hi and Lo registers in MIPS** combine to act as 64-bit register for multiply and divide
- **Signed Divides:** Simplest is to remember signs, make positive, and complement quotient and remainder if necessary
  - **Note:** Dividend and Remainder must have same sign
  - **Note:** Quotient negated if Divisor sign & Dividend sign disagree  
e.g.,  $-7 \div 2 = -3$ , remainder =  $-1$
- **Possible for quotient to be too large:** if divide 64-bit integer by 1, quotient is 64 bits (“called saturation”)

# Summary

- **Bits have no inherent meaning: operations determine whether they are really ASCII characters, integers, floating point numbers**
- **Divide can use same hardware as multiply: Hi & Lo registers in MIPS**


# Designing a Single Cycle Datapath

# Outline


- **Where are we with respect to the BIG picture?**
- **The Steps of Designing a Processor**
- **Datapath and timing for Reg-Reg Operations**
- **Datapath for Logical Operations with Immediate**
- **Datapath for Load and Store Operations**
- **Datapath for Branch and Jump Operations**
 
# The Big Picture: Where are We Now?

- The Five Classic Components of a Computer



 
- Next Topic: Design a Single Cycle Processor


 
## The Big Picture: The Performance Perspective

- Performance of a machine is determined by:

- Instruction count
- Clock cycle time
- Clock cycles per instruction



- Processor design (datapath and control) will determine:

- Clock cycle time
- Clock cycles per instruction

- Single cycle processor:


- Advantage: One clock cycle per instruction
- Disadvantage: long cycle time

# How to Design a Processor: step-by-step

- 1. Analyze instruction set => datapath requirements
  - the meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
    - possibly more
  - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic
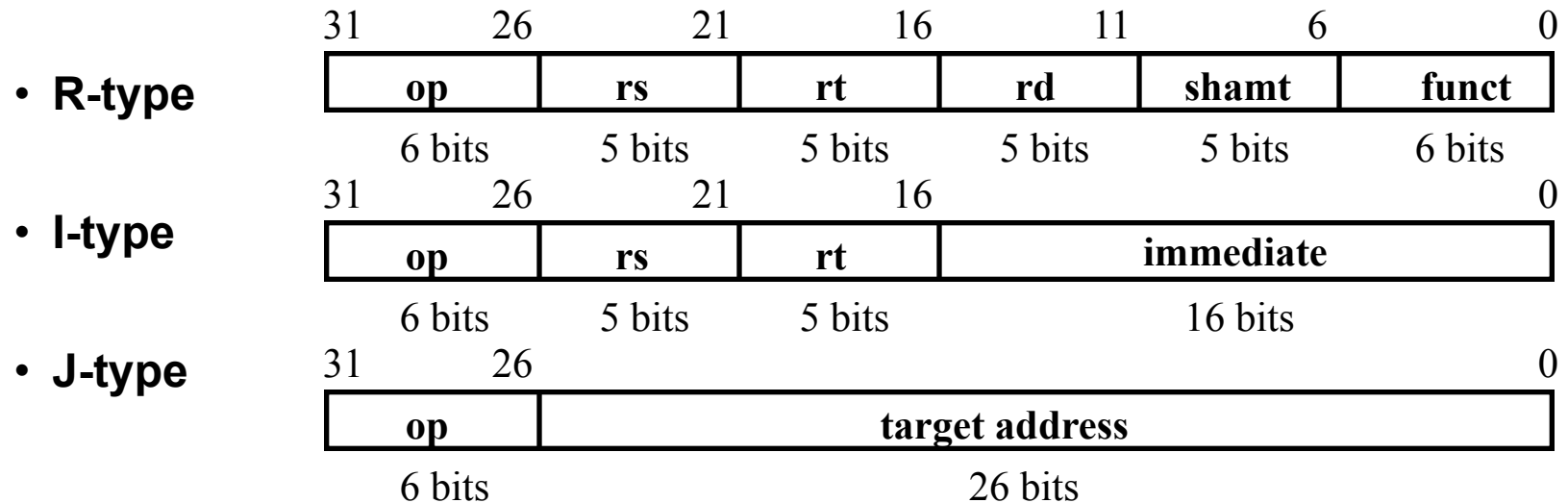
# The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
  - op: operation of the instruction
  - rs, rt, rd: the source and destination register specifiers
  - shamt: shift amount
  - funct: selects the variant of the operation in the “op” field
  - address / immediate: address offset or immediate value
  - target address: target address of the jump instruction



# Step 1a: The MIPS-lite Subset for today


## ◦ ADD and SUB

- addU rd, rs, rt
- subU rd, rs, rt

 


## ◦ OR Immediate:

- ori rt, rs, imm16

 


## ◦ LOAD and STORE Word

- lw rt, rs, imm16
- sw rt, rs, imm16

 

## ◦ BRANCH:

- beq rs, rt, imm16

 

# Logical Register Transfers

° RTL gives the meaning of the instructions

° All start by fetching the instruction

op | rs | rt | rd | shamt | funct = MEM[ PC ]

op | rs | rt | Imm16 = MEM[ PC ]

## inst            Register Transfers

**ADDU**       $R[rd] \leftarrow R[rs] + R[rt];$                        $PC \leftarrow PC + 4$

**SUBU**       $R[rd] \leftarrow R[rs] - R[rt];$                        $PC \leftarrow PC + 4$

**ORi**         $R[rt] \leftarrow R[rs] + \text{zero\_ext}(\text{Imm16});$                $PC \leftarrow PC + 4$

**LOAD**       $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})];$   $PC \leftarrow PC + 4$

**STORE**      $\text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})] \leftarrow R[rt];$   $PC \leftarrow PC + 4$

**BEQ**                      if (  $R[rs] == R[rt]$  ) then  $PC \leftarrow PC + 4 + \text{sign\_ext}(\text{Imm16})$   
   else  $PC \leftarrow PC + 4$

## **Step 1: Requirements of the Instruction Set**


- **Memory**
  - **instruction & data**
- **Registers (32 x 32)**
  - **read RS**
  - **read RT**
  - **Write RT or RD**
- **PC**
- **Other elements to complete datapath**

## **Step 2: Components of the Datapath**


- **Combinational Elements**
- **Storage Elements**
  - **Clocking methodology**

# Combinational Logic Elements (Basic Building Blocks)


## ◦ Adder

 

## ◦ MUX

 

## ◦ ALU

 


# Storage Element: Register (Basic Building Block)
 
## ◦ Register

- Similar to the D Flip Flop except
  - N-bit input and output
  - Write Enable input


- Write Enable:
  - negated (0): Data Out will not change
  - asserted (1): Data Out will become Data In


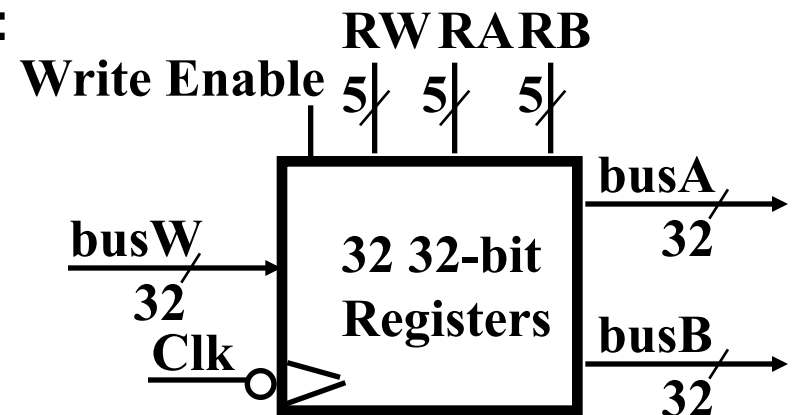
# Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:  
busA and busB
- One 32-bit input bus: busW



- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
  - RA or RB valid => busA or busB valid after “access time.”

# Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus


- **Clock input (CLK)**

 - The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
  - Address valid => Data Out valid after “access time.”





# Clocking Methodology

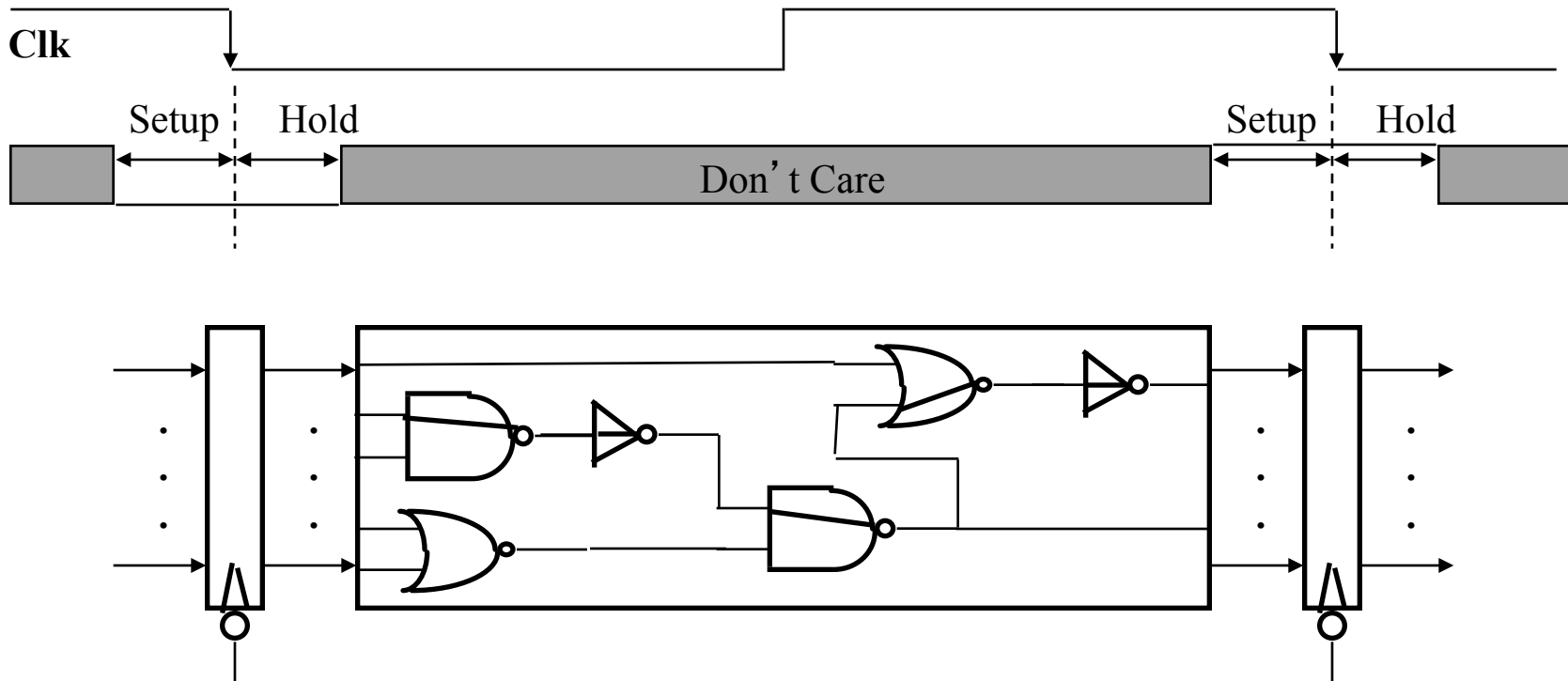


- ° All storage elements are clocked by the same clock edge
- °  $\text{Cycle Time} = \text{CLK-to-Q} + \text{Longest Delay Path} + \text{Setup} + \text{Clock Skew}$

## Step 3


- **Register Transfer Requirements**  
→ **Datapath Assembly**
- **Instruction Fetch**
- **Read Operands and Execute Operation**
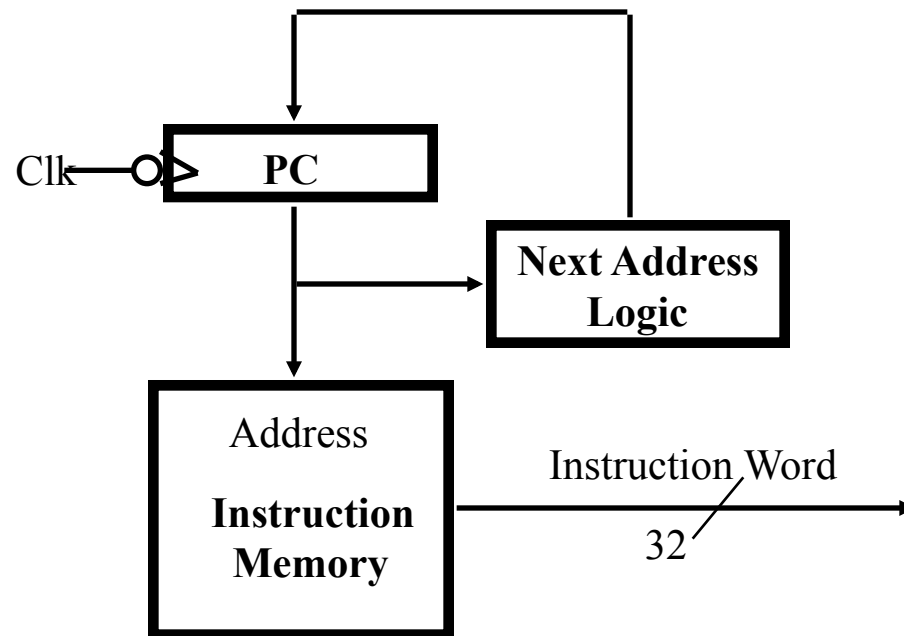
## 3a: Overview of the Instruction Fetch Unit

- The common RTL operations
  - Fetch the Instruction:  $\text{mem}[\text{PC}]$
  - Update the program counter:
    - Sequential Code:  $\text{PC} \leftarrow \text{PC} + 4$
    - Branch and Jump:  $\text{PC} \leftarrow \text{“something else”}$




# RTL: The ADD Instruction

 

◦ **add rd, rs, rt**

- **mem[PC]**                      **Fetch the instruction from memory**
- **$R[rd] \leftarrow R[rs] + R[rt]$**                       **The actual operation**
- **$PC \leftarrow PC + 4$**                       **Calculate the next instruction's address**

## RTL: The Subtract Instruction

 

◦ **sub rd, rs, rt**



- **mem[PC]**                      **Fetch the instruction from memory**
- **R[rd] <- R[rs] - R[rt]**                      **The actual operation**
- **PC <- PC + 4**                      **Calculate the next instruction's address**

## 3b: Add & Subtract



°  $R[rd] \leftarrow R[rs] \text{ op } R[rt]$

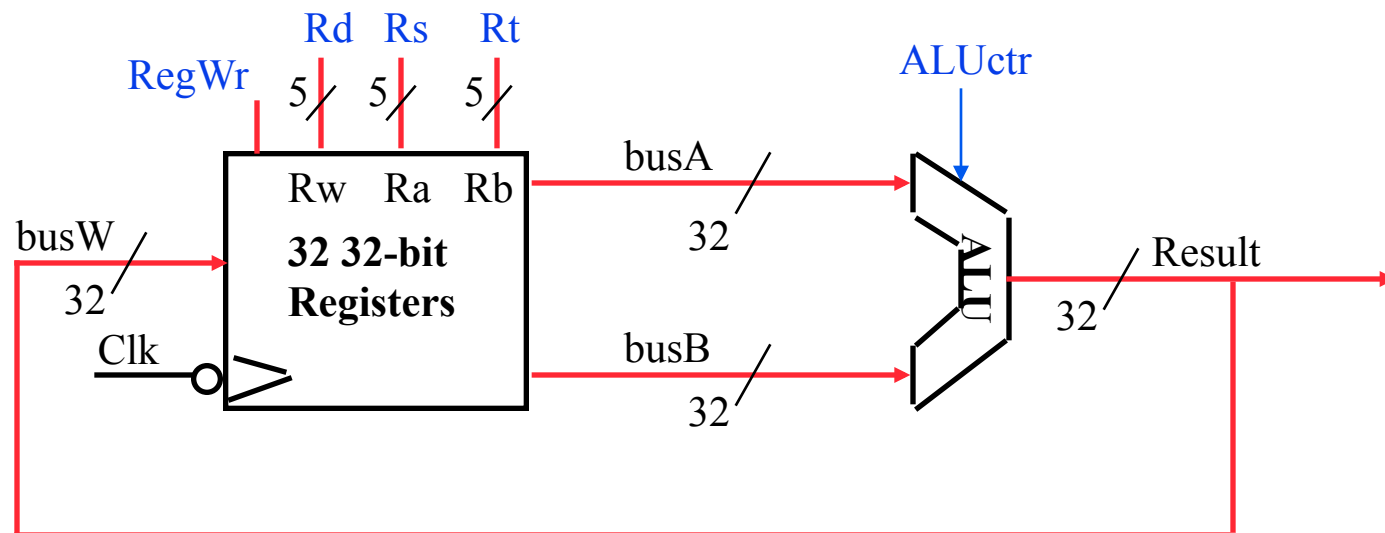 Example: addU rd, rs, rt


- Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
- ALUctr and RegWr: control logic after decoding the instruction



# Register-Register Timing

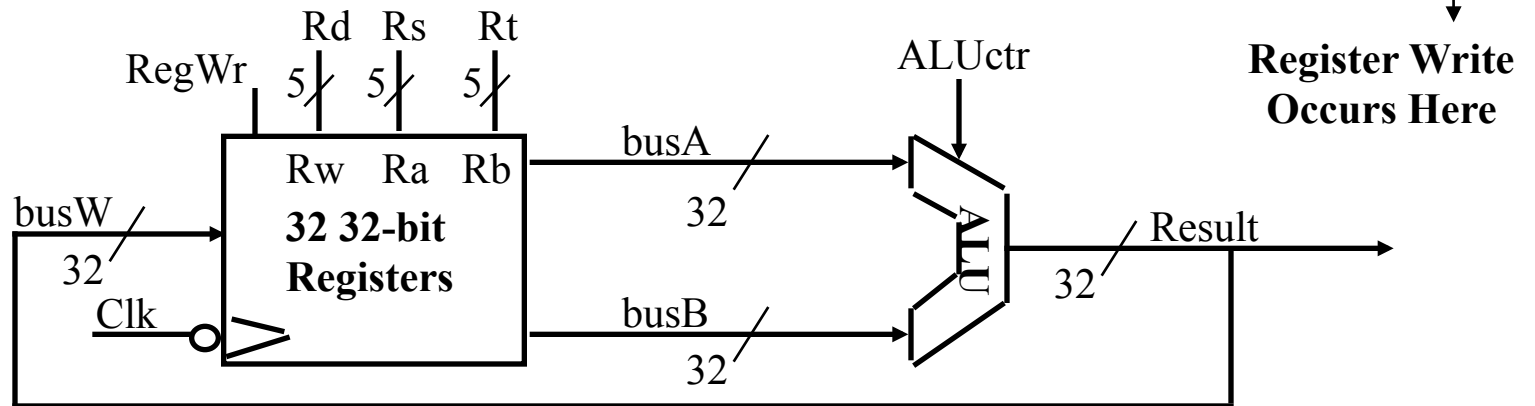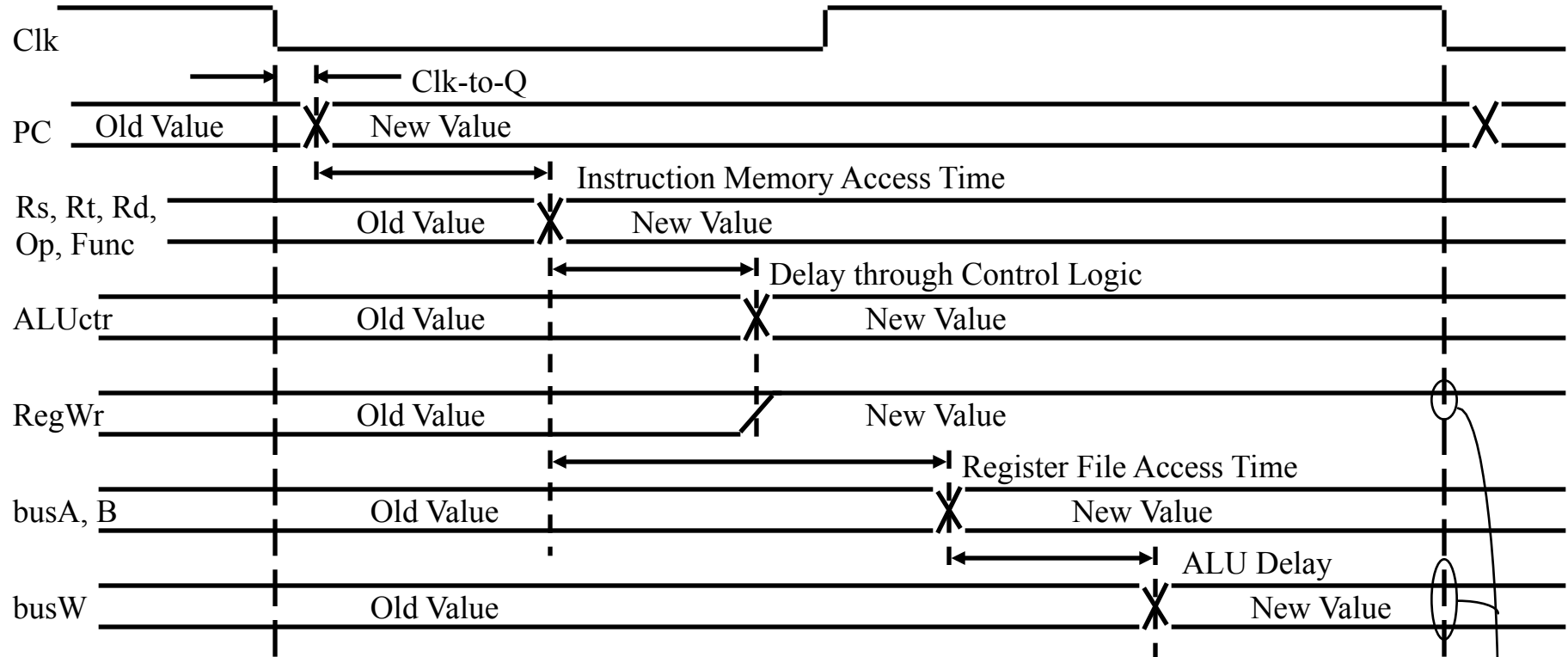


## RTL: The OR Immediate Instruction

 

- **ori rt, rs, imm16**


 
- **mem[PC]**                      **Fetch the instruction from memory**
- **R[rt] <- R[rs] or ZeroExt(imm16)**  
  **The OR operation**
- **PC <- PC + 4**                 **Calculate the next instruction's address**





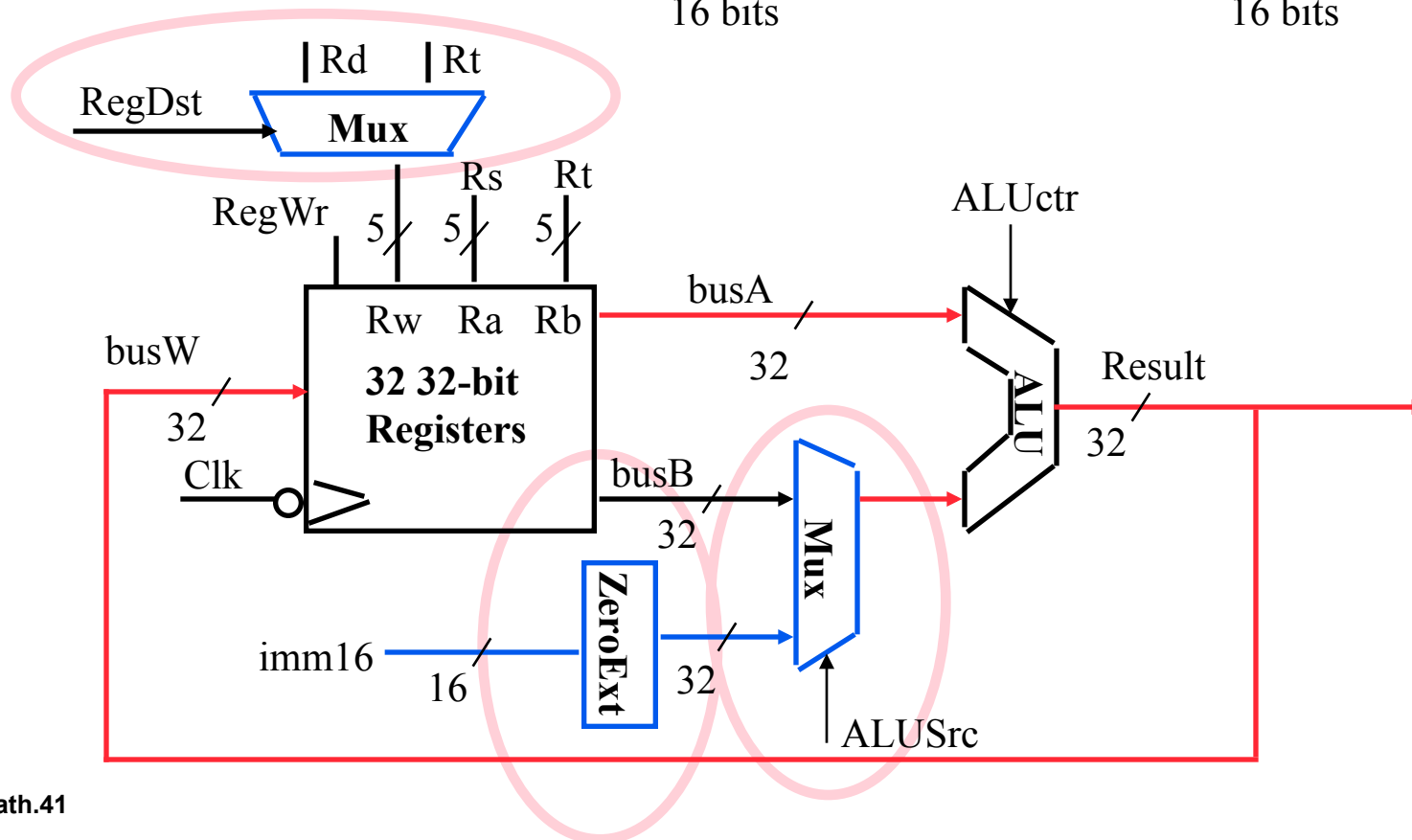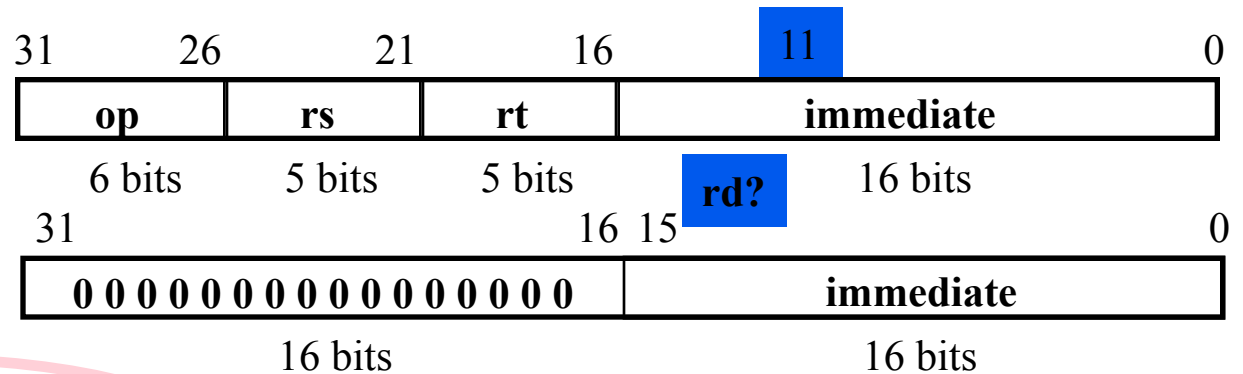
### 3c: Logical Operations with Immediate

°  $R[\text{rt}] \leftarrow R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



# RTL: The Load Instruction

 

• mem[PC]      **Fetch the instruction from memory**

• Addr <- R[rs] + SignExt(imm16)


**Calculate the memory address**

R[rt] <- Mem[Addr]

**Load the data into the register**



• PC <- PC + 4

 **Calculate the next instruction's address**



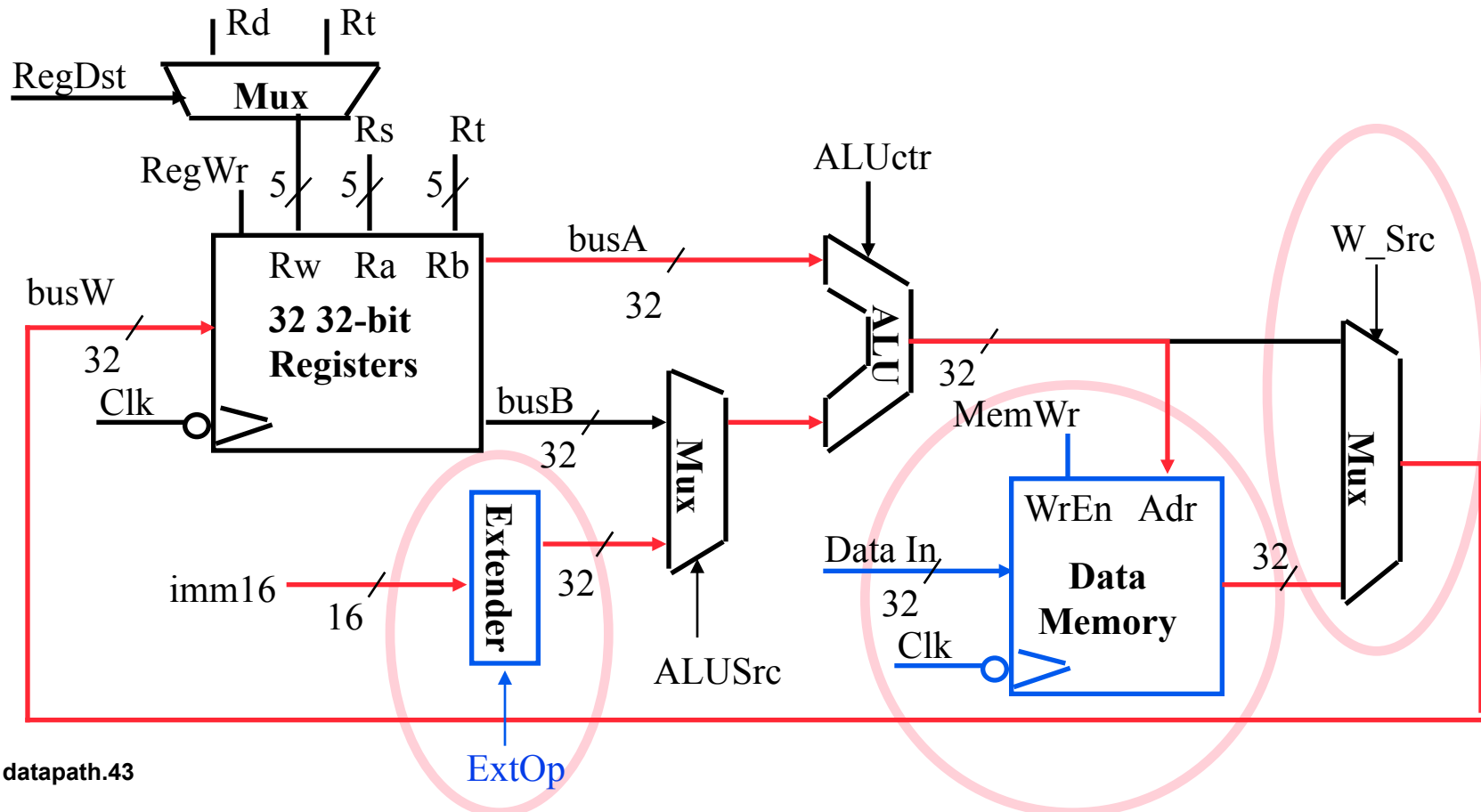
 
## 3d: Load Operations

°  $R[\underline{rt}] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$       Example: `lw rt, rs, imm16`


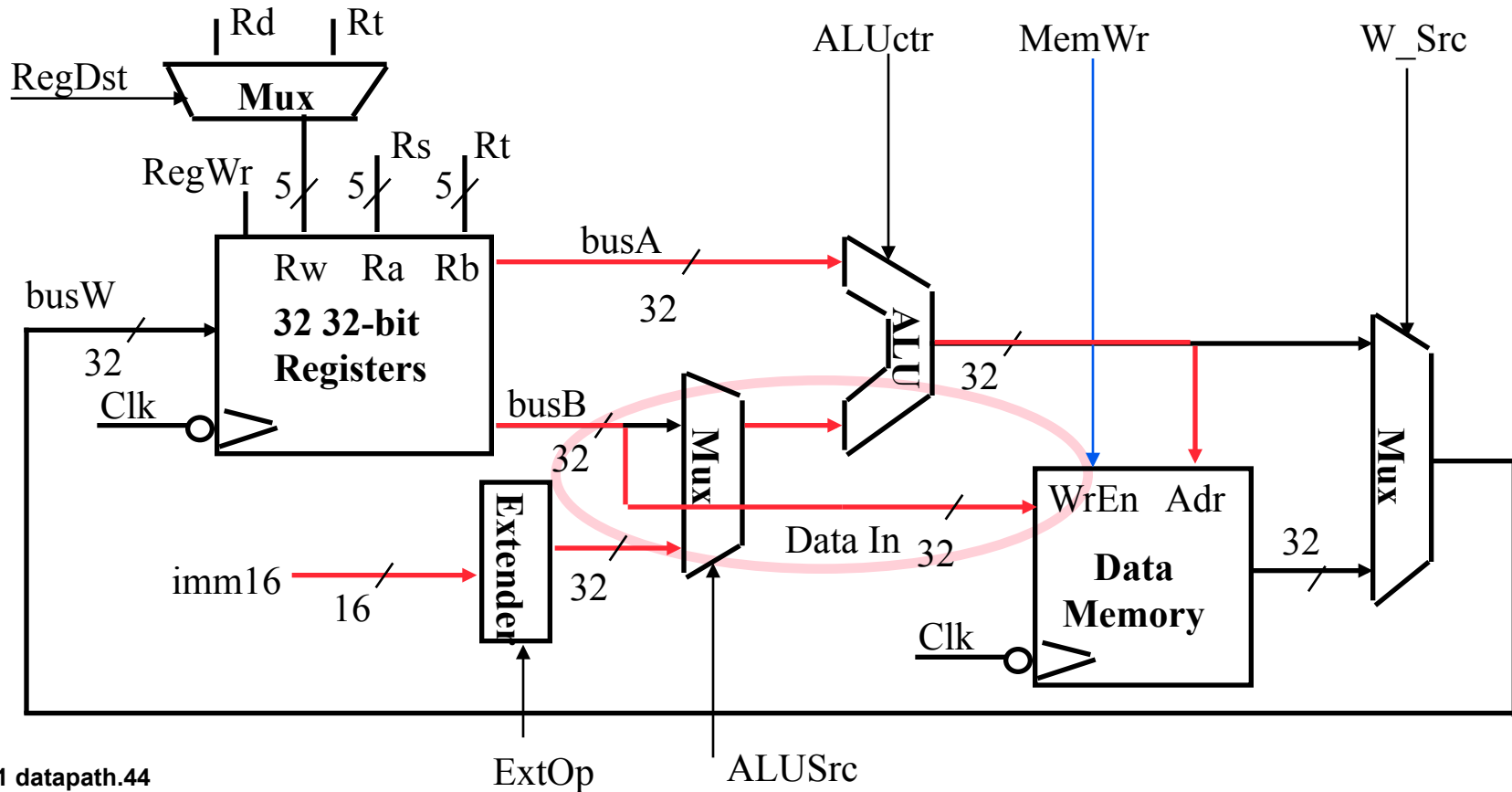 
## 3e: Store Operations

- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow R[\text{rt}]$     Example: `sw rt, rs, imm16`



# Summary

## ◦ 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

## ◦ MIPS makes it easier

- Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates

## ◦ Single cycle datapath

=> CPI=1, CCT (clock cycle time) = long

## ◦ Next time: other insts and implementing control