

Student ID: \_\_\_\_\_

Name: \_\_\_\_\_

Northwestern University  
Department of Electrical Engineering and Computer Science  
EECS 361 Computer Architecture

Instructor: Gokhan Memik (memik@eecs.northwestern.edu)

Quiz #3

1) What is the most important disadvantage of a ripple-carry adder?

It is slow: the carry out signal of a bit is used as an input in the next bit, generating a long critical path.

2) What does “successive refinement” mean?

Successive refinement is a design technique where first an inefficient version is developed, which is then optimized in successive steps.

3) What is the logic equation to create the  $C_{in}$  to the second bit (in other words,  $C_1$ ) in the carry-lookahead adder? Note that you can use  $A_0$ ,  $B_0$ , and  $C_0$  in the equation.

$$C_1 = (A_0 \text{ and } B_0) \text{ or } ((A_0 \text{ xor } B_0) \text{ and } C_0)$$