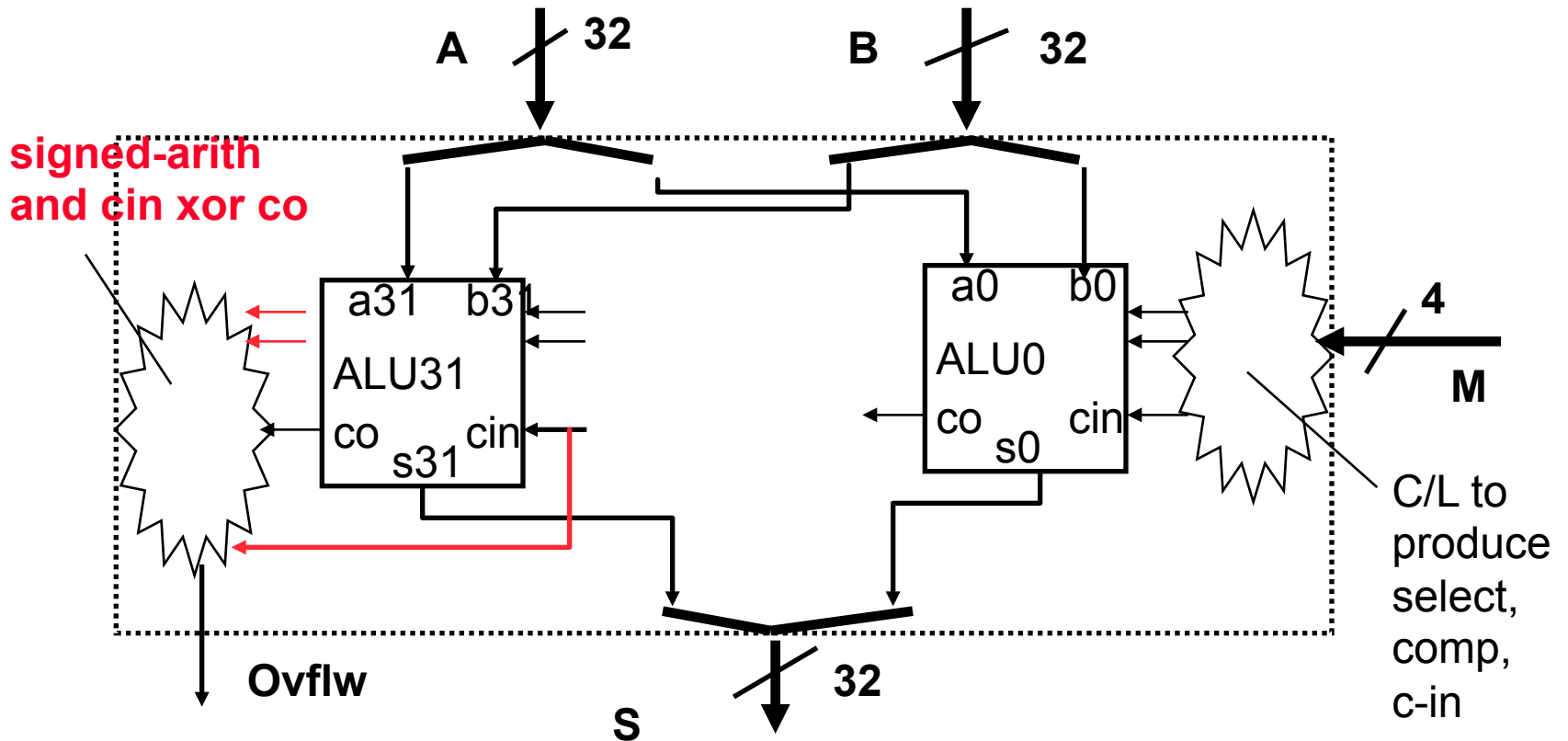


Computer Architecture
EECS 361
Lecture 6: ALU Design

Review: ALU Design

- Bit-slice plus extra on the two ends
- Overflow means number too large for the representation
- Carry-look ahead and other adder tricks



Review: Elements of the Design Process

- **Divide and Conquer (e.g., ALU)**
 - **Formulate a solution in terms of simpler components.**
 - **Design each of the components (subproblems)**
- **Generate and Test (e.g., ALU)**
 - **Given a collection of building blocks, look for ways of putting them together that meets requirement**
- **Successive Refinement (e.g., multiplier, divider)**
 - **Solve "most" of the problem (i.e., ignore some constraints or special cases), examine and correct shortcomings.**
- **Formulate High-Level Alternatives (e.g., shifter)**
 - **Articulate many strategies to "keep in mind" while pursuing any one approach.**
- **Work on the Things you Know How to Do**
 - **The unknown will become “obvious” as you make progress.**

Outline of Today' s Lecture

- Deriving the ALU from the Instruction Set
- Multiply

MIPS arithmetic instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comments</i>
add	add \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; exception possible
add immediate	addi \$1,\$2,100	$\$1 = \$2 + 100$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; no exceptions
add imm. unsign. no exceptions	addiu \$1,\$2,100		$\$1 = \$2 + 100$ + constant;
multiply	mult \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit unsigned product
divide	div \$2,\$3	Lo = $\$2 \div \3 ,	Lo = quotient, Hi = remainder
			Hi = $\$2 \bmod \3
divide unsigned	divu \$2,\$3	Lo = $\$2 \div \3 ,	Unsigned quotient & remainder
			Hi = $\$2 \bmod \3
Move from Hi	mfhi \$1	$\$1 = \text{Hi}$	Used to get copy of Hi
Move from Lo	mflo \$1	$\$1 = \text{Lo}$	Used to get copy of Lo

MIPS logical instructions


<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \sim\$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable

Additional MIPS ALU requirements

- **Xor, Nor, Xorl**
=> Logical XOR, logical NOR or use 2 steps: $(A \text{ OR } B) \text{ XOR } 1111\dots1111$
- **Sll, Srl, Sra**
=> Need left shift, right shift, right shift arithmetic by 0 to 31 bits
- **Mult, MultU, Div, DivU**
=> Need 32-bit multiply and divide, signed and unsigned

Add XOR to ALU

- Expand Multiplexor

 


MULTIPLY (unsigned)

- Paper and pencil example (unsigned):

Multiplicand	1000
Multiplier	1001
	<hr/>
	1000
	0000
	0000
	<hr/>
Product	01001000


- m bits \times n bits = $m+n$ bit product
- Binary makes it easy:
 - 0 \Rightarrow place 0 (0 \times multiplicand)
 - 1 \Rightarrow place a copy (1 \times multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement

Unsigned Combinational Multiplier

 

- Stage i accumulates $A * 2^i$ if $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?


How does it work?

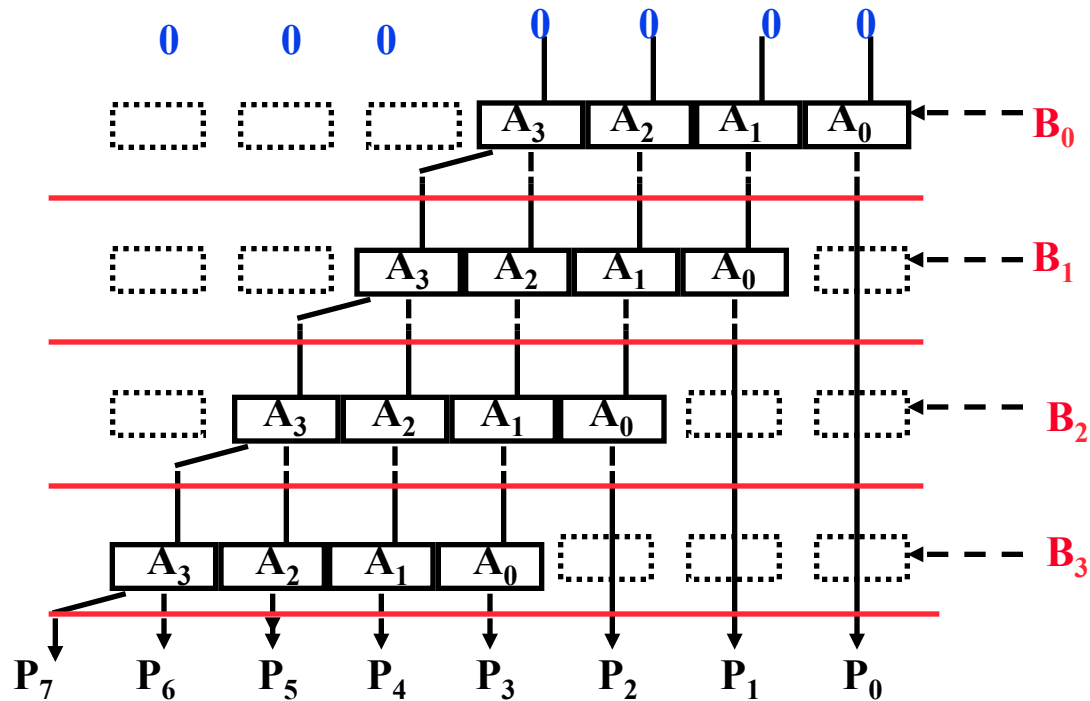

- at each stage shift A left (x 2)
- use next bit of B to determine whether to add in shifted multiplicand
- accumulate 2n bit partial product at each stage

Unsigned shift-add multiplier (version 1)

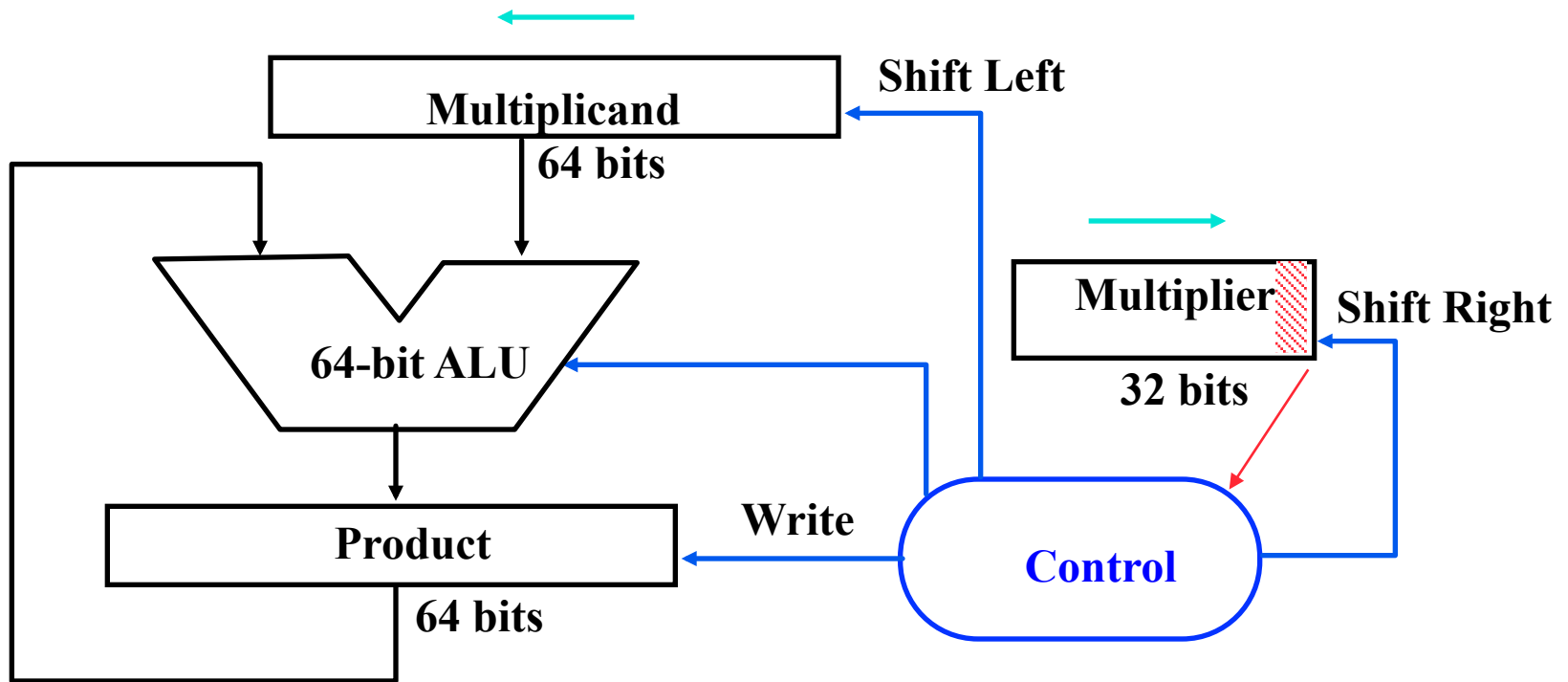
- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

Multiply Algorithm Version 1

Product	Multiplier	Multiplicand
0000 0000	0011	0000 0010
0000 0010	0001	0000 0100
0000 0110	0000	0000 1000
0000 0110		

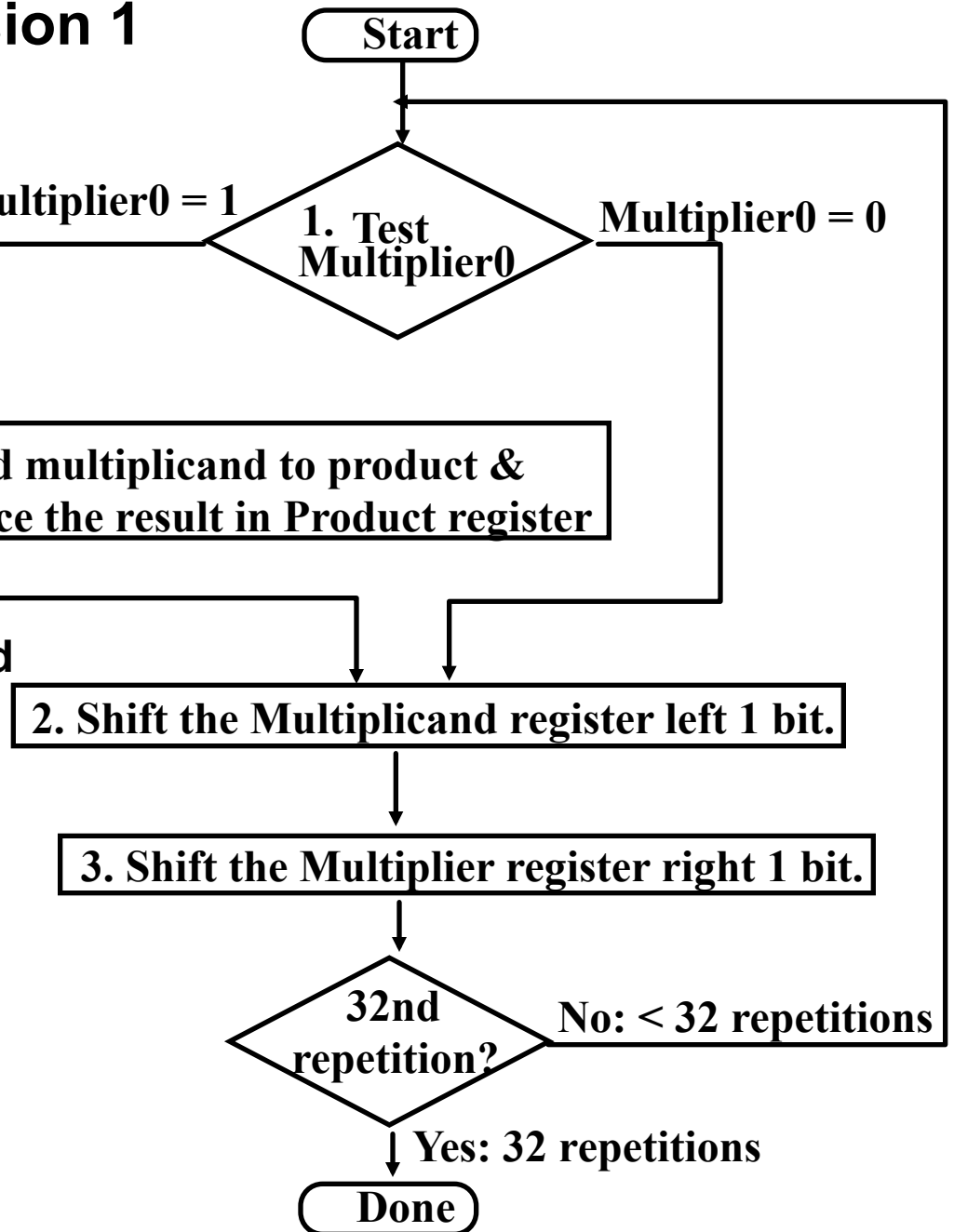


Observations on Multiply Version 1


- 1 clock per step $\Rightarrow 32 \times 3 = \sim 100$ clocks per multiply
 - Ratio of multiply frequency to add 1:5 to 1:100
 - Remember Amdahl's Law
- 1/2 bits in multiplicand always 0
 \Rightarrow 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted
 \Rightarrow least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

MULTIPLY HARDWARE Version 2

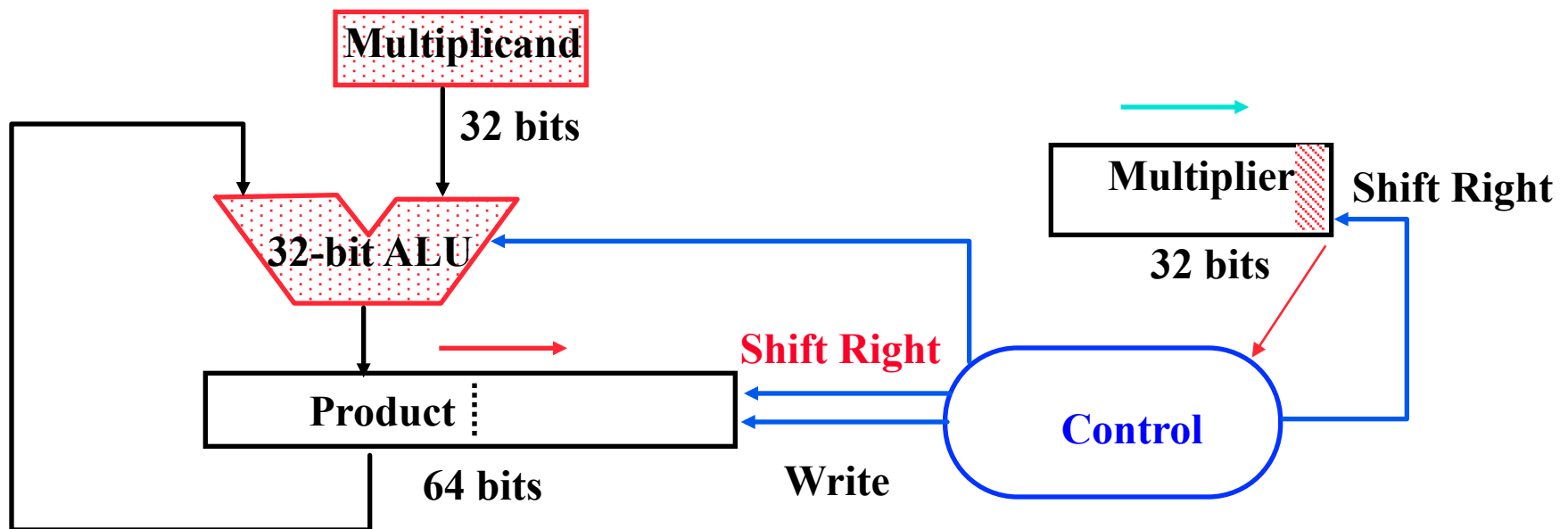
- **32-bit** Multiplicand reg, **32-bit** ALU, 64-bit Product reg, 32-bit Multiplier reg



Multiply Algorithm Version 2

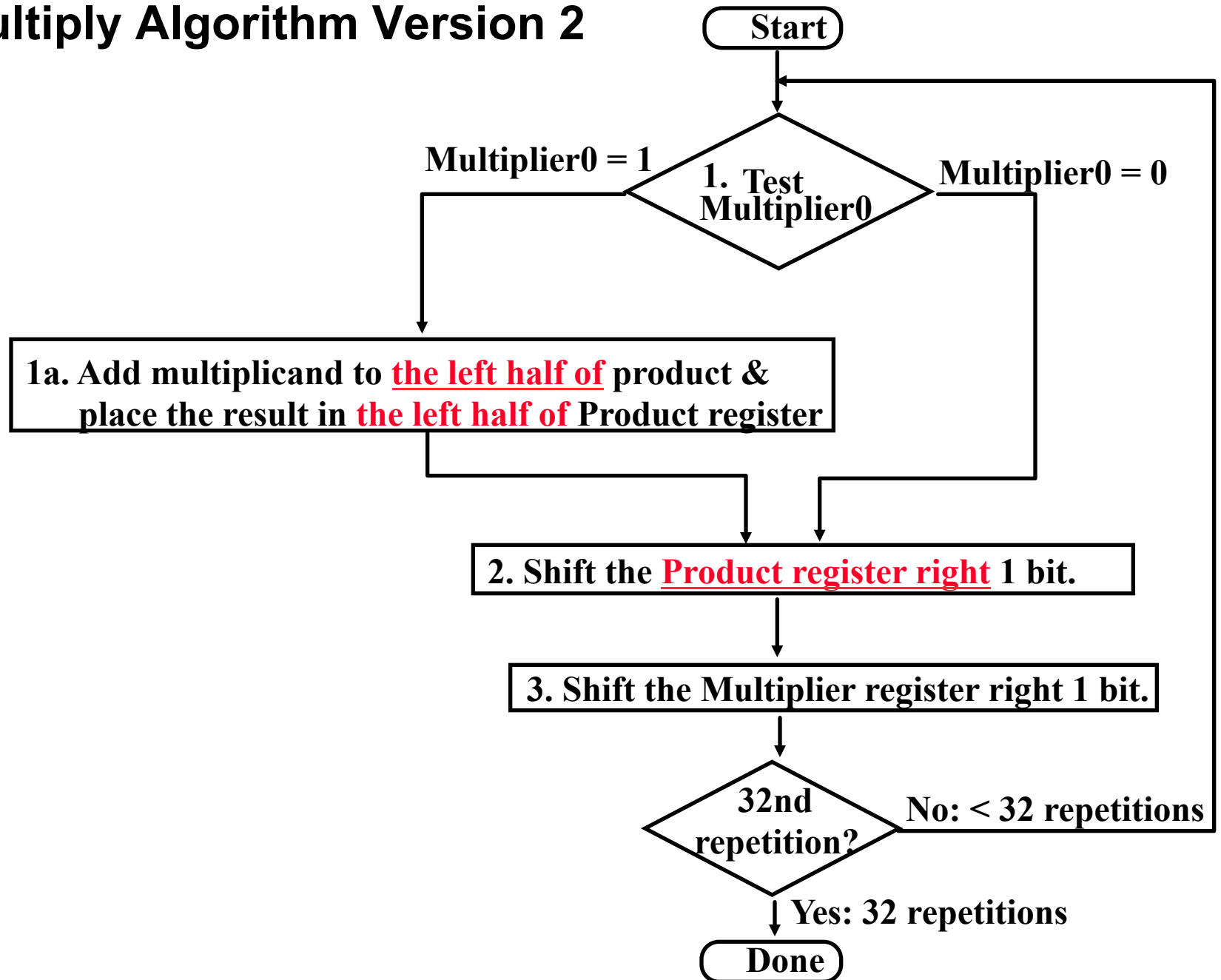


What's going on?

 

- Multiplicand stay's still and product moves right

Multiply Algorithm Version 2

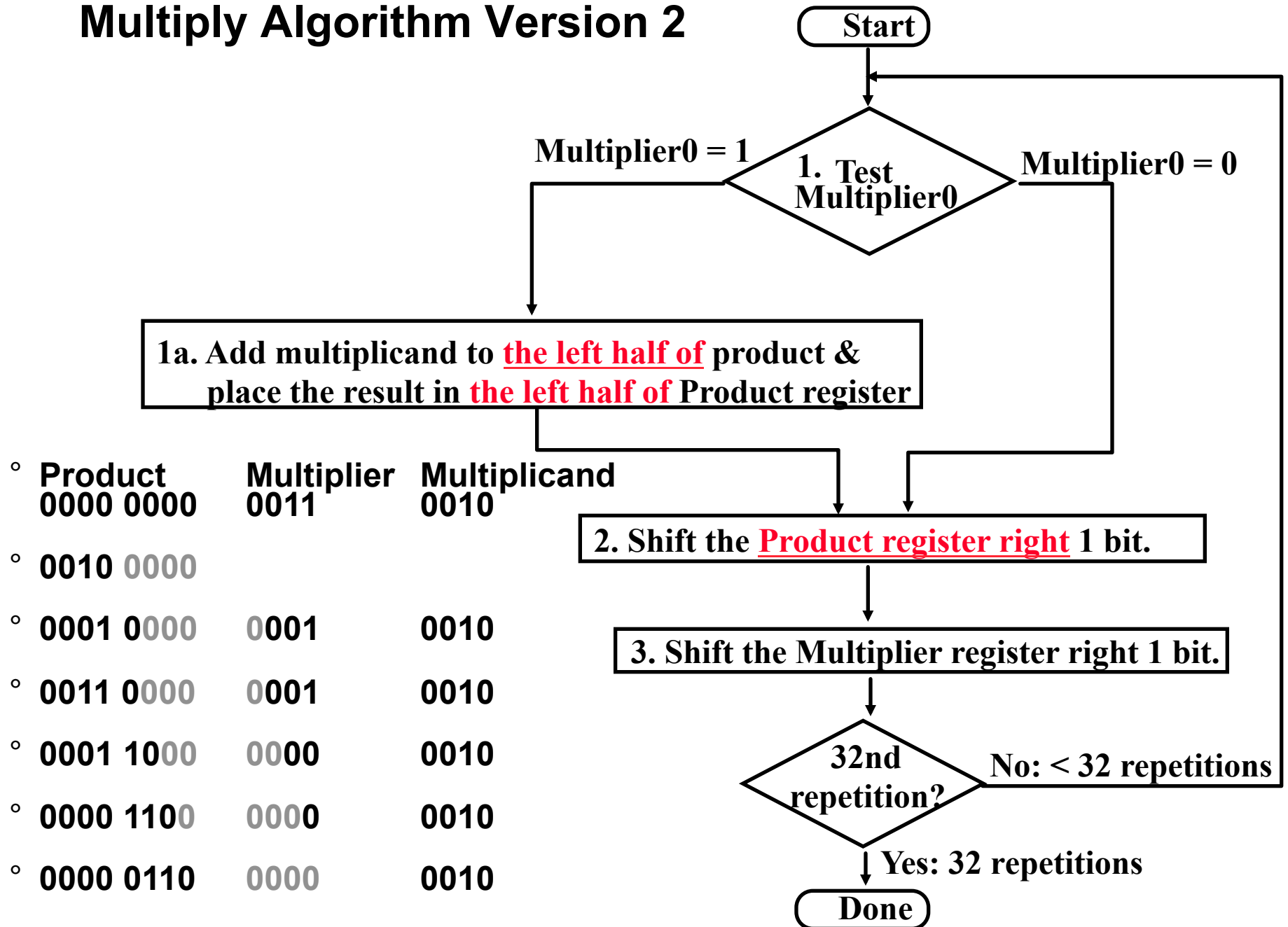


Observations on Multiply Version 2

- ° **Product register wastes space that exactly matches size of multiplier
=> combine Multiplier register and Product register**


MULTIPLY HARDWARE Version 3

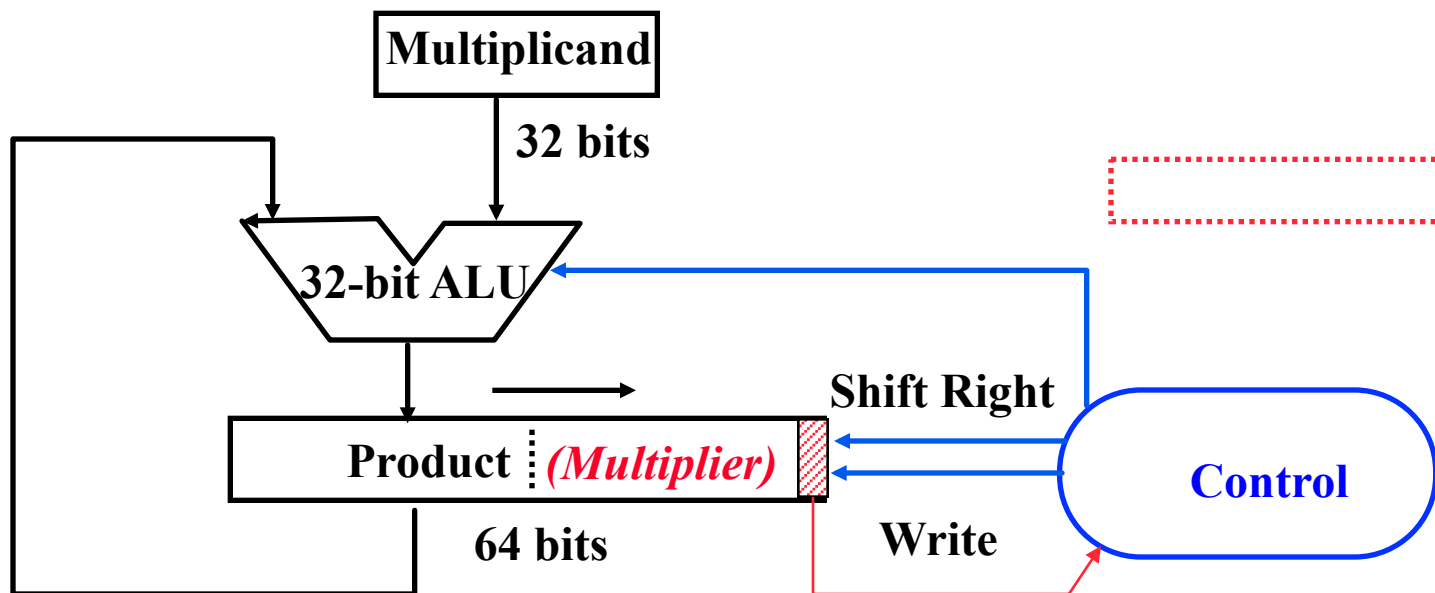- ° 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



Multiply Algorithm Version 3

Multiplicand Product
0010 0000 0011

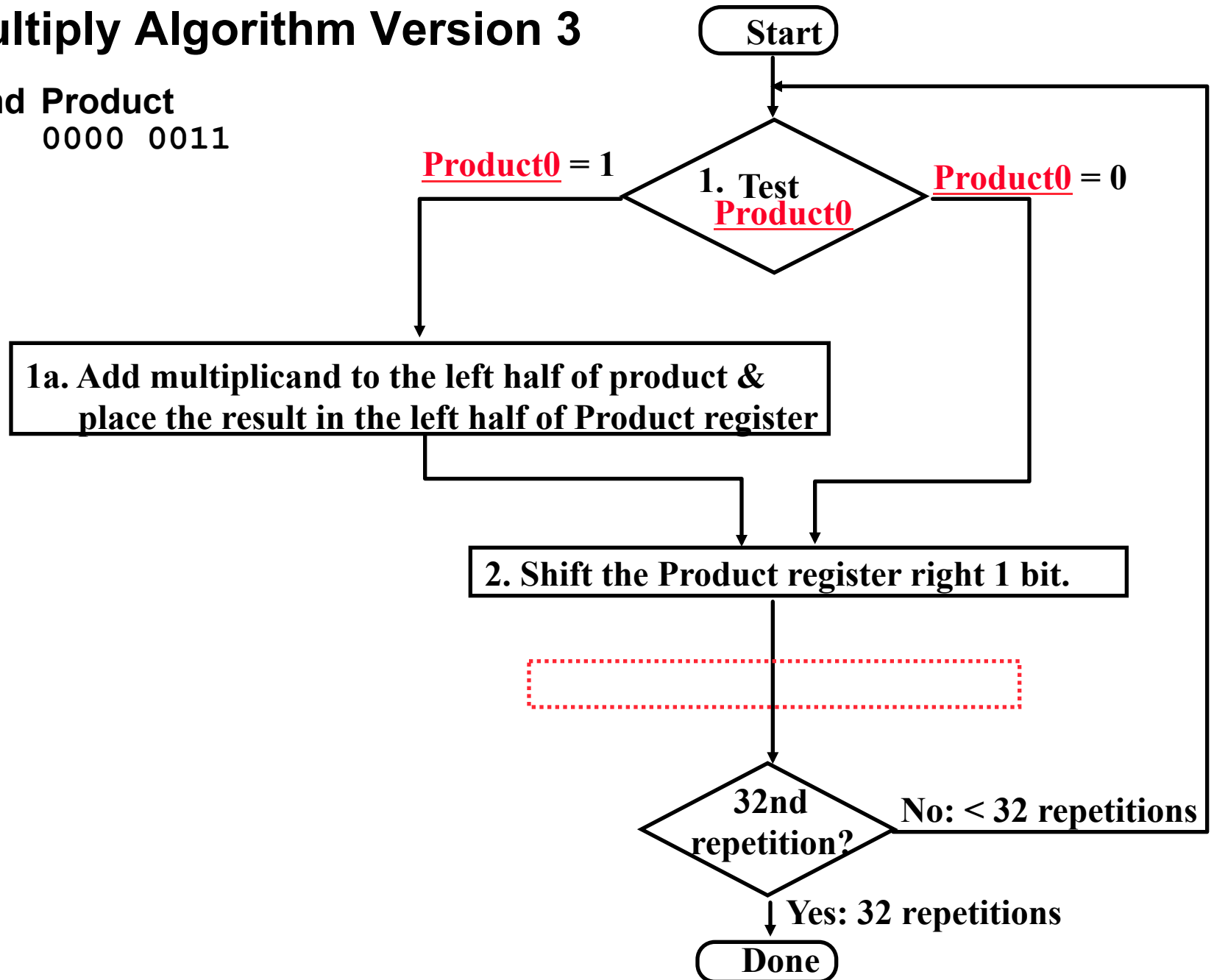

Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU
- **How can you make it faster?**
- What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - apply definition of 2's complement
 - need to sign-extend partial products and subtract at the end
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can handle multiple bits at a time

Motivation for Booth's Algorithm

- Example $2 \times 6 = 0010 \times 0110$:

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
<hr/>		
	00001100	


- ALU with add or subtract gets same result in more than one way:

6	= - 2 + 8	, or
0110	= - 0010 + 1000	

- Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one. For example

	0010	
x	0110	
+	0000	shift (0 in multiplier)
-	0010	sub (first 1 in multiplier)
+	0000	shift (middle of string of 1s)
+	0010	add (prior step had last 1)
<hr/>		
	00001100	

Booth's Algorithm Insight

 

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	00011 <u>11</u> 000
0	1	End of a run of 1s	00 <u>01</u> 111000
0	0	Middle of a run of 0s	0 <u>00</u> 1111000

Originally for Speed since shift faster than add for his machine

Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one

Booths Example (2 x 7)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 0111 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 0111 0	shift P (sign ext)
1b.	0010	1111 0 011 1	11 -> nop, shift
2.	0010	1111 10 01 1	11 -> nop, shift
3.	0010	1111 110 0 1	01 -> add
4a.	0010	+ 0010 0001 110 0 1	shift
4b.	0010	0000 1110 0	done

Booths Example (2 x -3)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	$\begin{array}{r} + 1110 \\ \hline 1110 \text{ 1101 } 0 \end{array}$	shift P (sign ext)
1b.	0010	$\begin{array}{r} 1111 \text{ 0110 } 1 \\ + 0010 \\ \hline \end{array}$	01 -> add
2a.		0001 0 110 1	shift P
2b.	0010	$\begin{array}{r} 0000 \text{ 1011 } 0 \\ + 1110 \\ \hline \end{array}$	10 -> sub
3a.	0010	1110 10 11 0	shift
3b.	0010	1111 010 1 1	11 -> nop
4a		1111 010 1 1	shift
4b.	0010	1111 1010 1	done

Booth's Algorithm - Summary

1. Depending on the current and previous bits, do one of the following:

- 00: a. Middle of a string of 0s, so no arithmetic operations.
- 01: b. End of a string of 1s, so add the multiplicand to the left half of the product.
- 10: c. Beginning of a string of 1s, so subtract the multiplicand from the left half of the product.
- 11: d. Middle of a string of 1s, so no arithmetic operation.

2. As in the previous algorithm, shift the Product register right (arith) 1 bit.


MIPS logical instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \mid \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \mid \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 \mid 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \sim\$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable


Shifters

Three different kinds:

logical-- value shifted in is always "0"

 

 arithmetic-- on right shifts, sign extend




rotating-- shifted out bits are wrapped around (not in MIPS)




Note: these are single bit shifts. A given instruction might request 0 to 31 bits to be shifted!

Combinational Shifter from MUXes

Basic Building Block

 


8-bit right shifter

 

- What comes in the MSBs?
- How many levels for 32-bit shifter?
- What if we use 4-1 Muxes ?

 General Shift Right Scheme using 16 bit example



If added Right-to-left connections could support Rotate (not in MIPS but found in other ISAs)

Summary

- **Instruction Set drives the ALU design**
- **Multiply: successive refinement to see final design**
 - **32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register**
 - **Booth's algorithm to handle signed multiplies**
- **There are algorithms that calculate many bits of multiply per cycle**
- **What's Missing from MIPS is Divide & Floating Point Arithmetic**