 


Lecture 16

Memory



Adapted from slides originally developed by Profs. Hardavellas, Hill, Falsafi, Marculescu, Patterson, Rutenbar and Vijaykumar of Northwestern, Carnegie Mellon, Purdue, UC-Berkley, UWisconsin


Review: Improving Cache Performance

- ▶ **Boiled it all down to three basic types of optimizations**
 - ▷ O1: Reducing the cache miss rate
 - ▷ Larger blocks, higher associativity, victim caches, prefetching
 - ▷ O2: Reducing the cache miss penalty
 - ▷ Loads before stores, sub-block, early restart, 2nd level caches
 - ▷ O3: Reducing the time to hit in the cache
 - ▷ Small caches, address translation

Today's Menu:

► Basic Memory Technology

- ▷ SRAM—Static RAM
- ▷ DRAM—Dynamic RAM

 

Random Access Memory (RAM) Technology

► Why do we need to know about RAM technology?

- ▷ Processor performance is usually limited by memory bandwidth
- ▷ As IC densities increase, lots of memory fits on processor chip
- ▷ Tailor on-chip memories to very specific needs
 - ▷ Instruction cache
 - ▷ Data cache
 - ▷ Write buffer

► What makes RAM different from a bunch of flip-flops?

- ▷ **Density:** RAM is much more dense
- ▷ **Speed:** depending on how you design it, RAM may be fast, or very slow

Memory Technologies



► Random Access Memories

- ▷ **DRAM:** *Dynamic* Random Access Memory
 - ▷ High density, low power (0.1–0.5 W active, 0.25–10 mW standby), cheap, slow
 - ▷ Dynamic: needs to be “refreshed” regularly
 - ▷ Dynamic means “*I write a bit, and if I ignore it long enough, it will evaporate*”
 - ▷ Dynamic also means “*I read a bit, and then I have to write it back to make sure it is still correctly stored there*”
- ▷ **SRAM:** *Static* Random Access Memory
 - ▷ Low density (SRAM cell is 4-8x bigger than DRAM cell)
 - ▷ Fast (SRAM is 8-16x faster than DRAM)
 - ▷ High power, expensive
 - ▷ Static: content will last “forever”(until lose power)
 - ▷ Static means “*I write a bit, and it stays there. Period*”


► What gets used where (typically)?

- ▷ Main memory is **DRAM**: you need it big, so you need it cheap
- ▷ CPU cache memory is **SRAM**: you need it fast, so it's more expensive, so it's smaller than you would usually want due to resource limitations

Illustrative Analogy...

  


 **This is your CPU's
Main memory subsystem
You want it big**



**This is your CPU
You want it fast**


Memory 2D Array Issues: Decoders

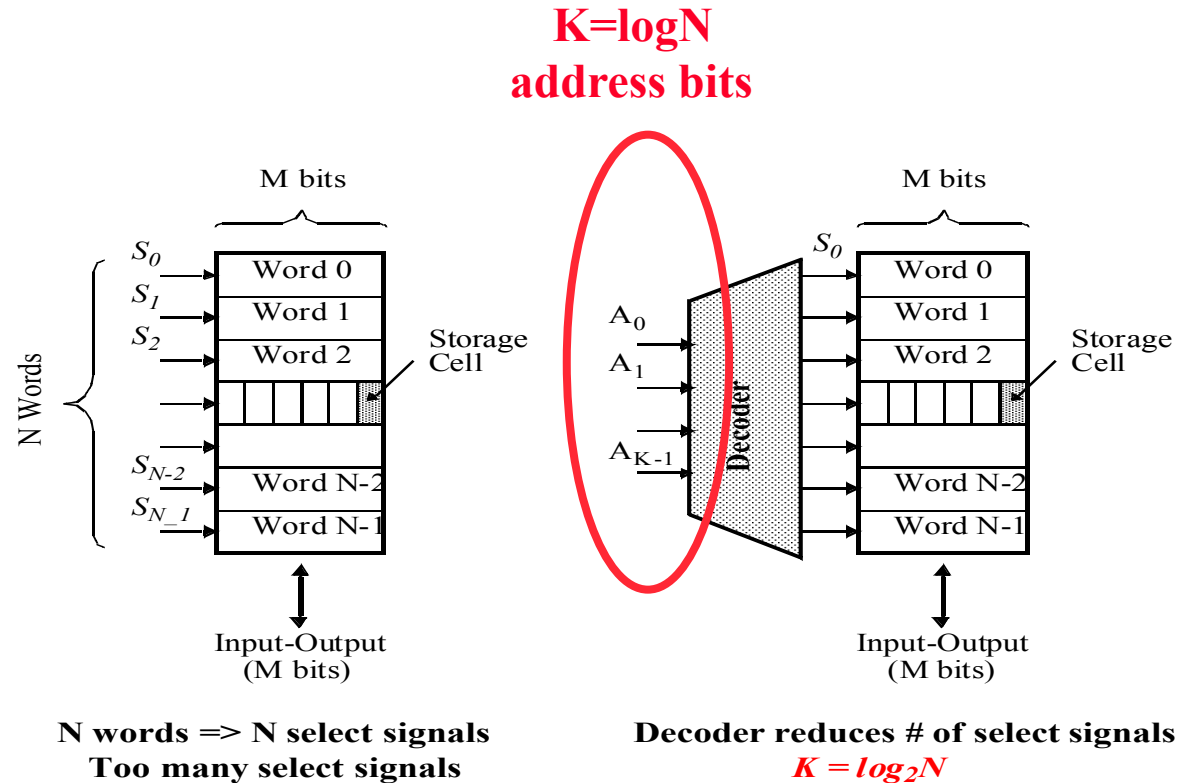

Array-Structured Memory Architecture


- If you have 1M 1-bit words, you *don't* want a 1M x 1 2D array

Problem: ASPECT RATIO or HEIGHT >> WIDTH

 

Static RAM Cell: Circuits View (if you know ckts)

6-Transistor SRAM Cell

 


► Write:


1. Drive bit lines ($\text{bit} = x, \overline{\text{bit}} = \overline{x}$)
2. Select row (set word line to Vdd)

► Read:

 
1. Precharge bit and $\overline{\text{bit}}$ to Vdd
2. Select row
3. Cell pulls one line low
4. Special analog circuit called a “Sense amplifier” (or usually just “sense-amp”) on column detects the difference between bit and $\overline{\text{bit}}$, which denotes what we read



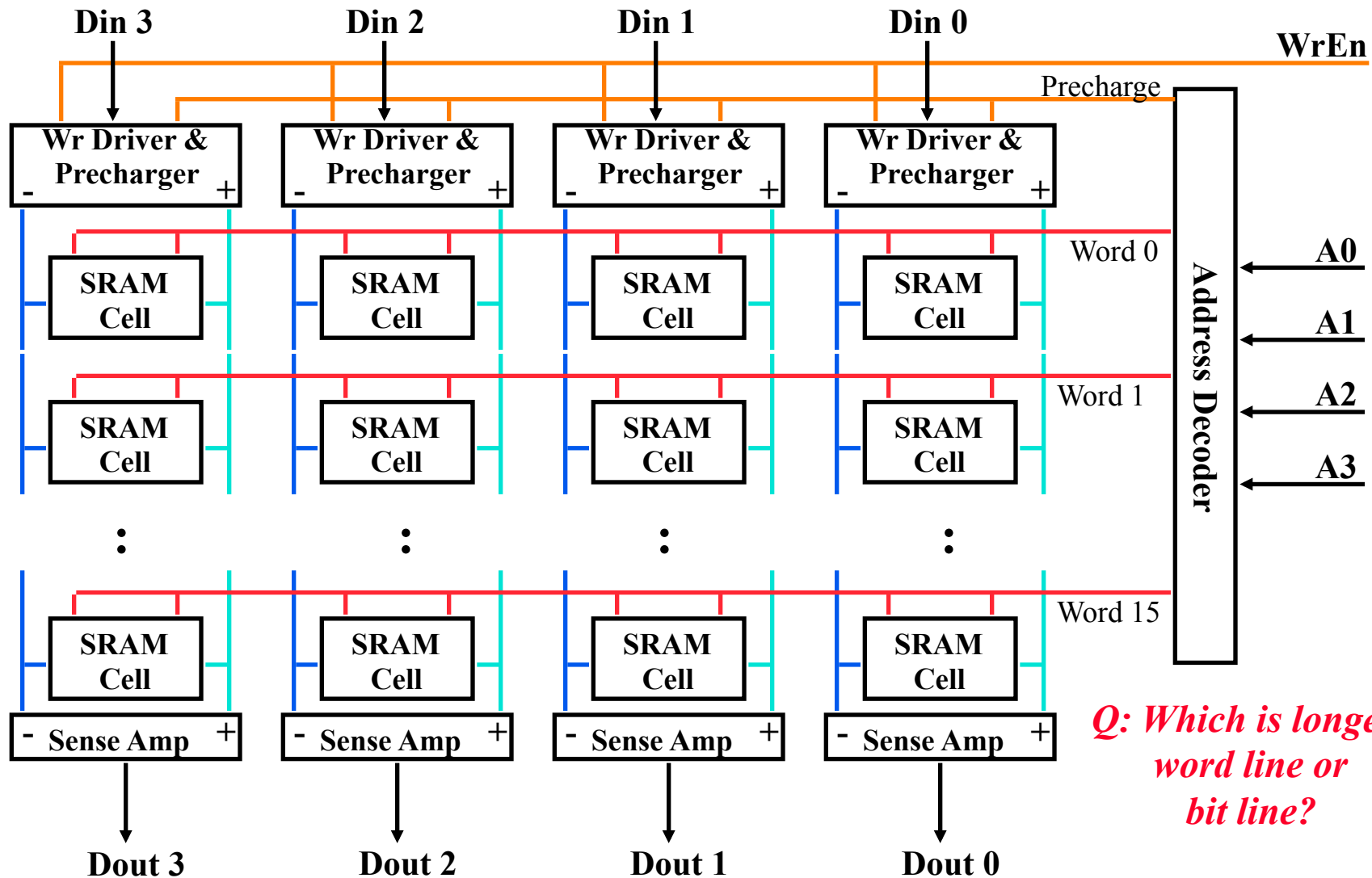Typical SRAM Organization: 16-word x 4-bit



Logic Diagram of a Typical SRAM

 


► Basic plumbing

- ▷ *WriteEnable* is usually active low (*WE_L*)
- ▷ *Din* and *Dout* are combined to save pins:

► A new signal, *OutputEnable* (*OE_L*) is needed


- ▷ *WE_L* is asserted (Low), *OE_L* is de-asserted (High)
 - ▷ *D* serves as the data **input** pins
- ▷ *WE_L* is de-asserted (High), *OE_L* is asserted (Low)
 - ▷ *D* is the data **output** pins
- ▷ Both *WE_L* and *OE_L* are asserted:
 - ▷ Result is **unknown**. **Don't do that!!!**

Typical SRAM Timing

 


Write Timing:

Read Timing:

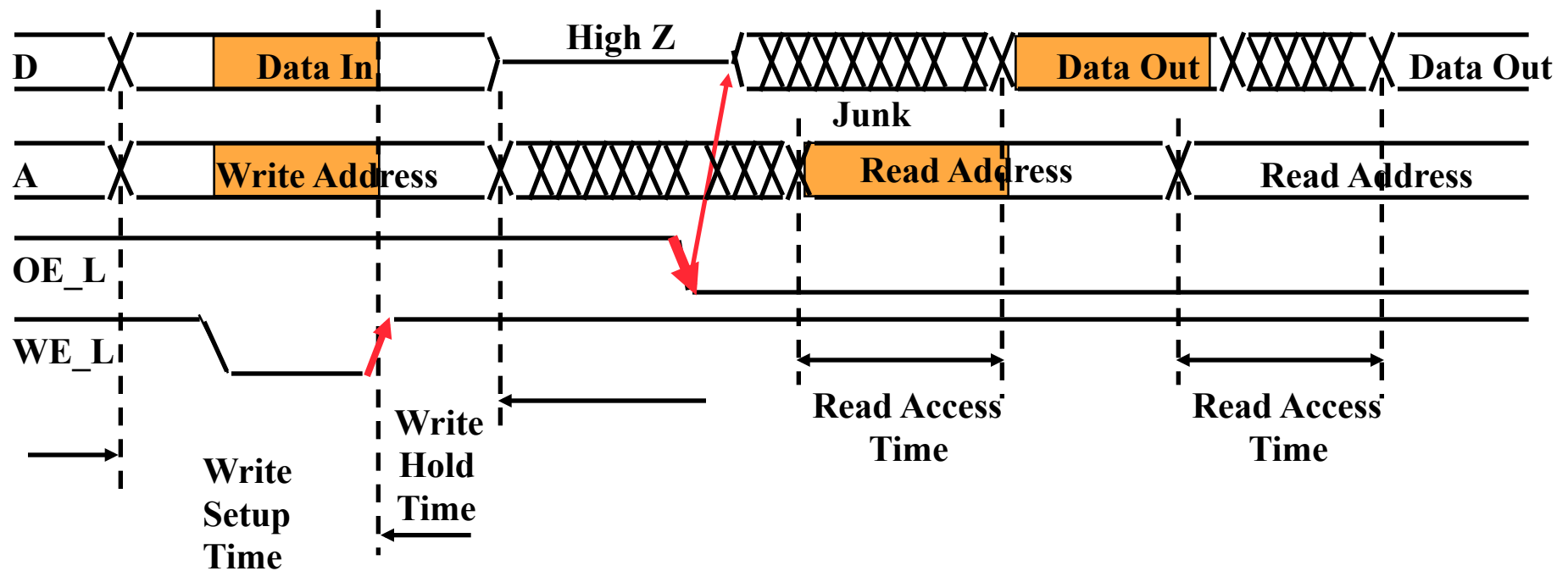

Problems with SRAM

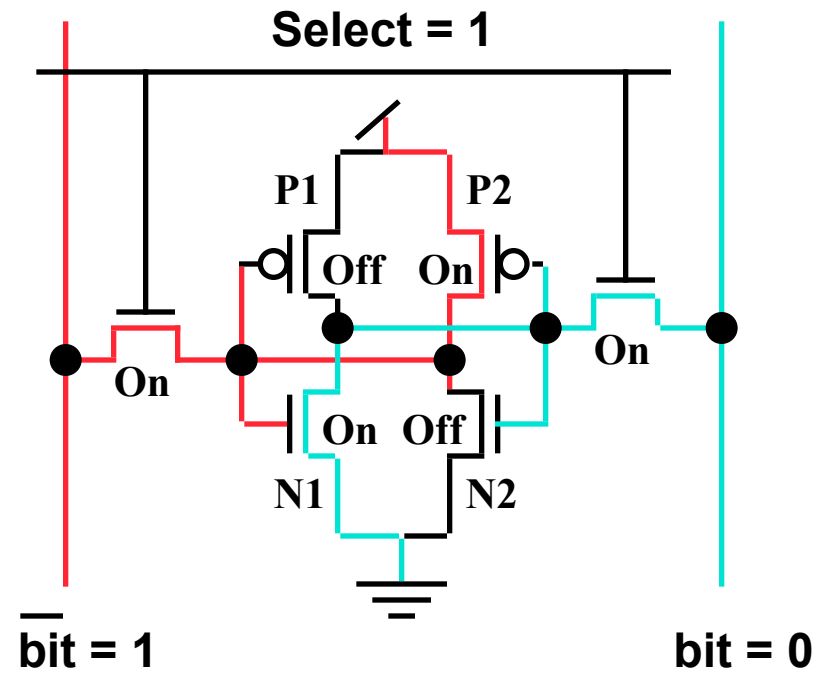

► Issues

- ▷ 6 transistors is a lot of area, if want millions of stored bits
- ▷ It's fast, and it's static (ie, it's cross-coupled like a flip-flop, so it regenerates state from inputs)...
- ▷ ...but, as a result, it's electrically "on" all the time (depending on ckt design)
- ▷ Can be a major power dissipation issue

Other option: 1-Transistor Memory Cell (DRAM)

► Write:


- ▷ 1. Drive bit line
- ▷ 2. Select row (called word-line)

► Read:

- ▷ 1. Precharge bit line to $V_{dd}/2$
- ▷ 2. Select row
- ▷ 3. Cell and bit line share charges
 - ▷ Very small voltage changes on the bit line
- ▷ 4. Sense (fancy sense amp)
 - ▷ Can detect changes of ~ 1 million electrons
- ▷ 5. Write: restore the value

► Refresh

 - ▷ 1. Just do a dummy read to every cell.



Closer Look at DRAM Cell


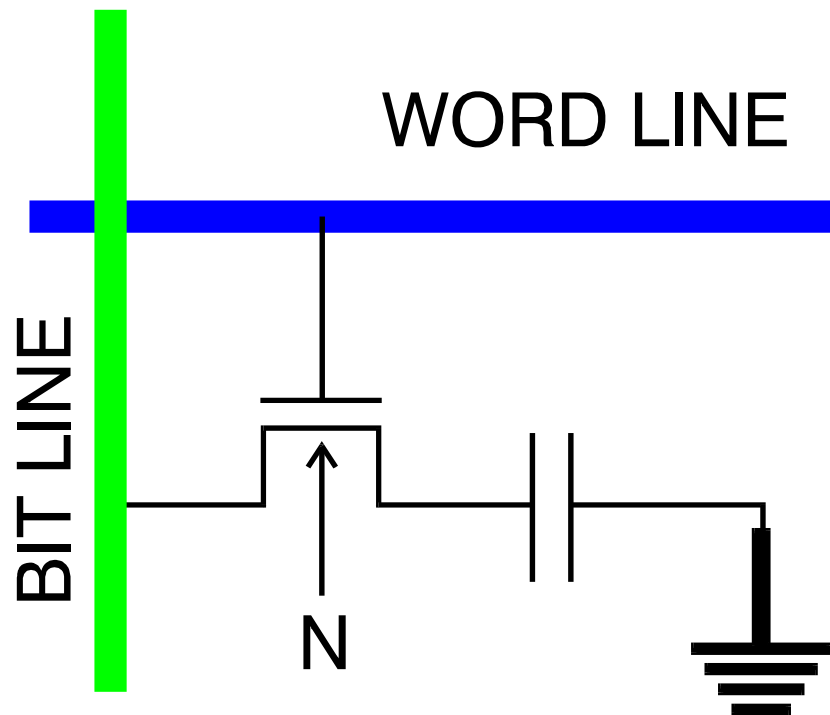


Figure 1: IBM Trench Capacitor Memory Cell

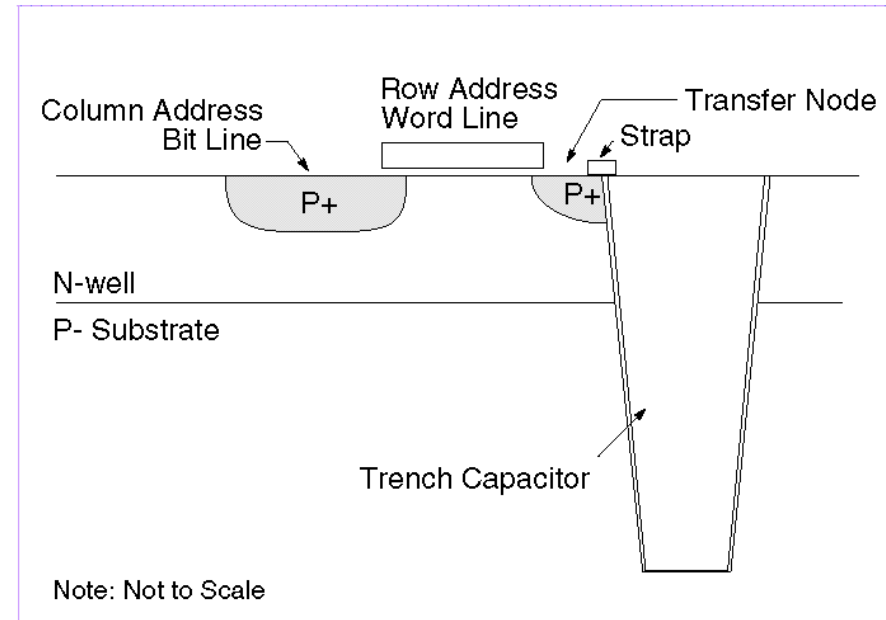

Problem is: you want more and more bits/chip.




So, each bit gets smaller and smaller.

So, the capacitor gets smaller and smaller.


But, the capacitor needs physical area to store enough charge.

Solution: dig a hole in silicon, called a “*trench*”

DRAMs with Stack Capacitors

   


Classical DRAM Organization (square)

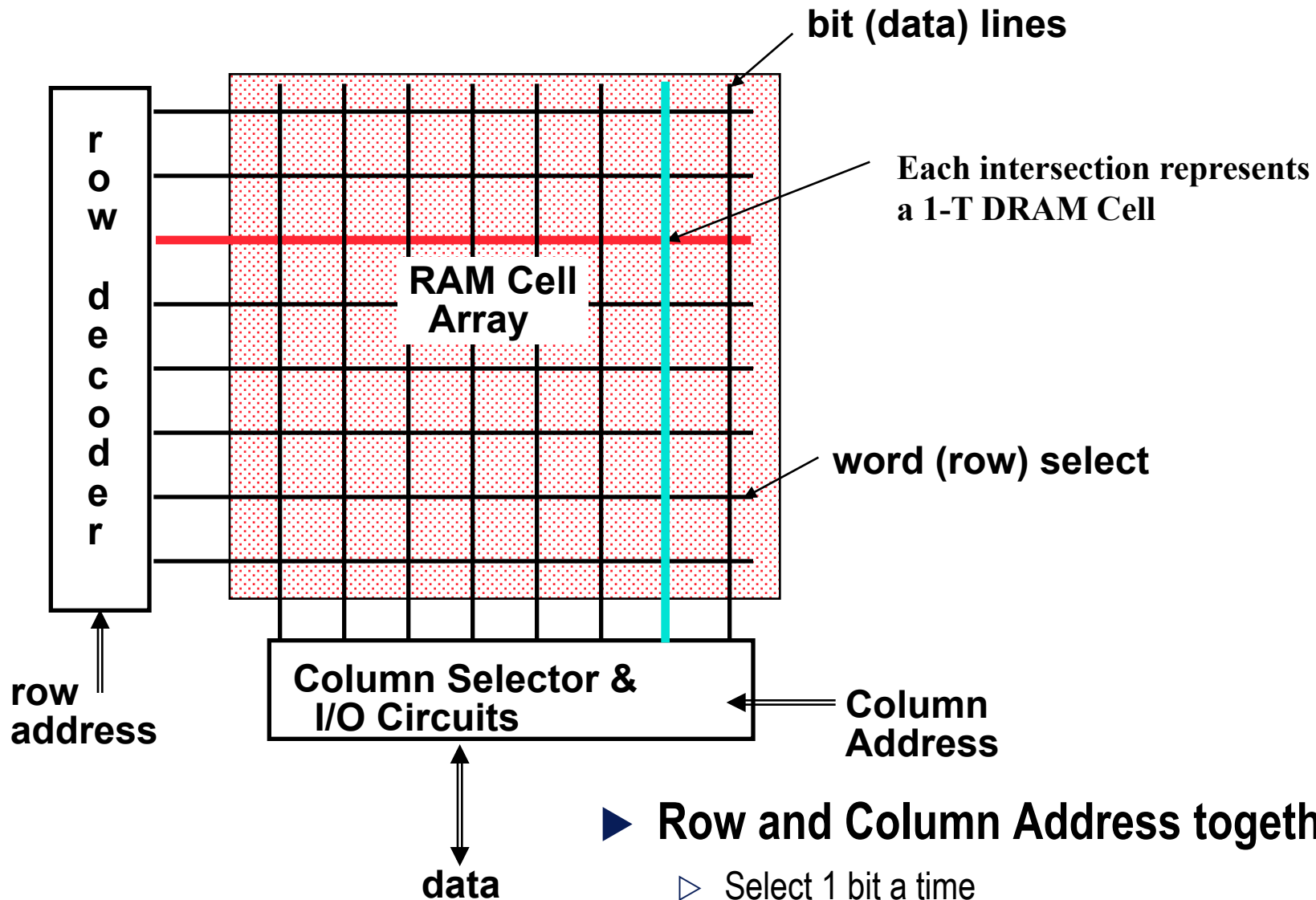


Typical DRAM Organization

 - ▶ **Typical DRAMs: access multiple bits in parallel**
 - ▷ Example: 2 Mb DRAM = 256K x 8 = 512 rows x 512 cols x 8 bits
 - ▷ Row and column addresses are applied to all 8 planes in parallel



Logic Diagram of a Typical DRAM

 

► Control Signals (*RAS_L*, *CAS_L*, *WE_L*, *OE_L*)

- ▷ All active low

► *Din* and *Dout* are combined (*D*):

- ▷ *WE_L* is asserted (Low), *OE_L* is disasserted (High): *D* serves as the data **input** pin
- ▷ *WE_L* is disasserted (High), *OE_L* is asserted (Low): *D* is the data **output** pin


► Row and column addresses *share the same pins* (*A*)

- ▷ *RAS_L* goes low: Pins *A* are latched in as row address
- ▷ *CAS_L* goes low: Pins *A* are latched in as column address
- ▷ *RAS/CAS* edge-sensitive

} **Weird
but common
on DRAMs...**

DRAM Write Timing

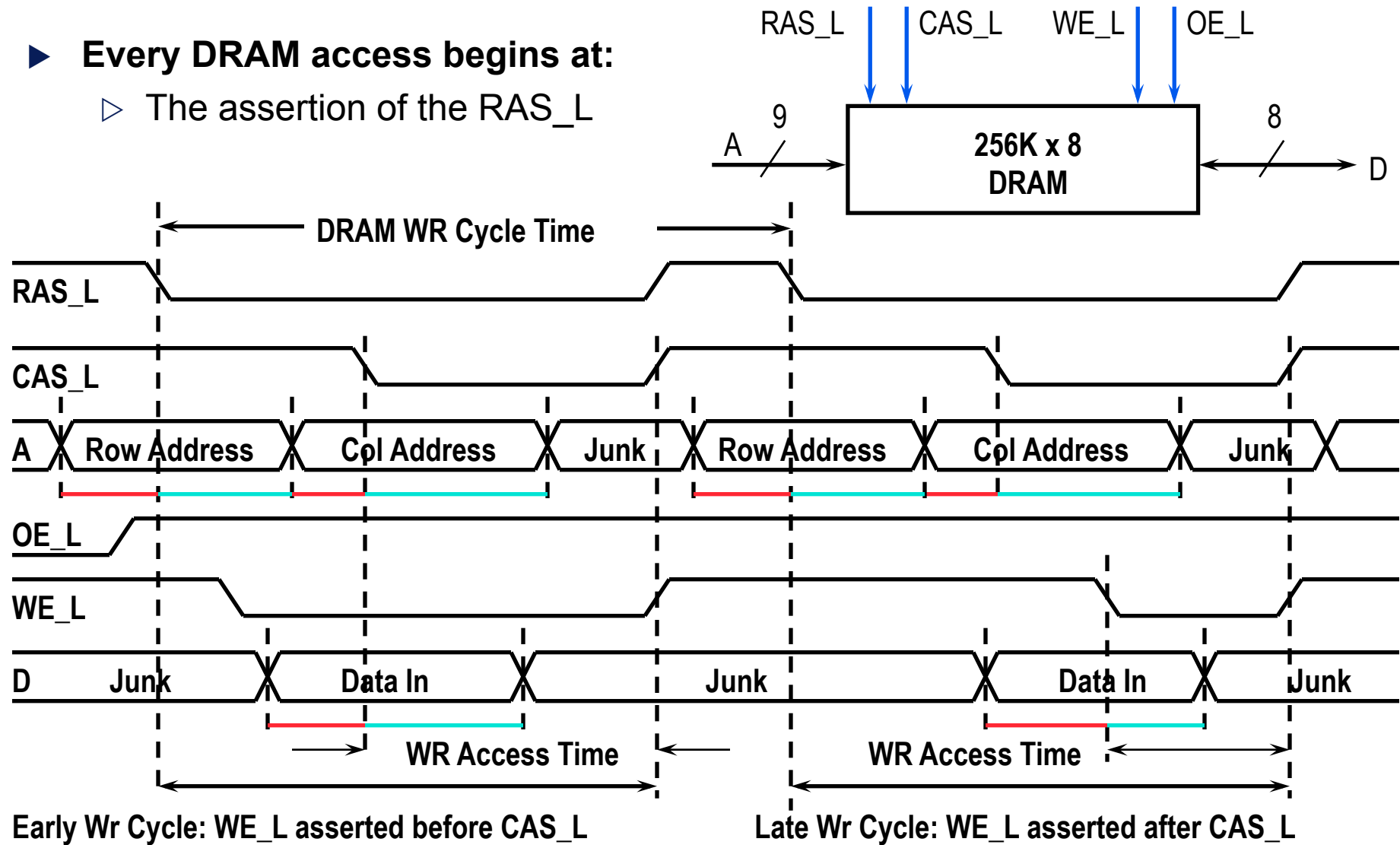
- Every DRAM access begins at:
 - ▷ The assertion of the RAS_L



DRAM Read Timing

- **Every DRAM access begins at:**

- The assertion of the RAS_L

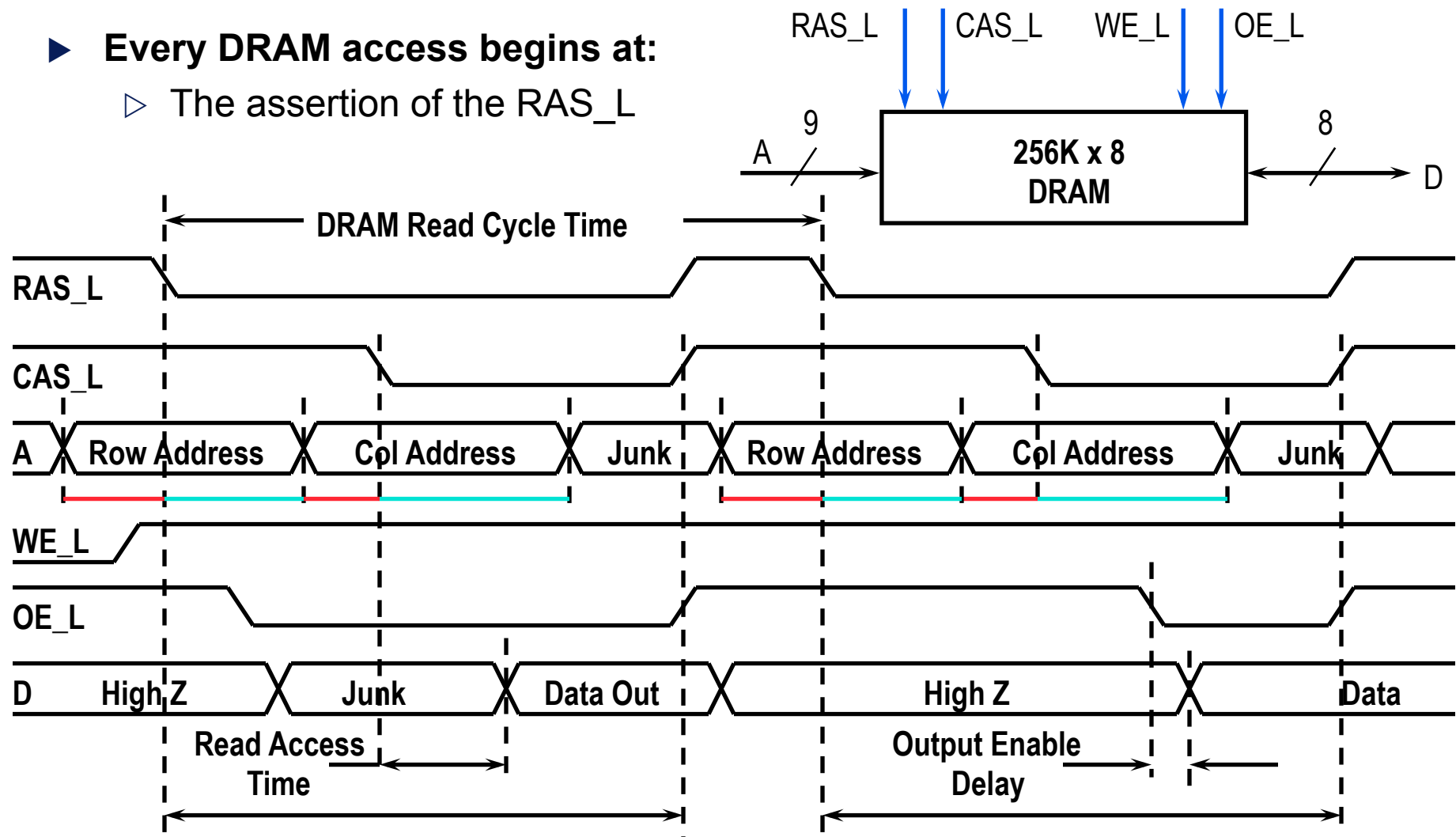

Early Read Cycle: OE_L asserted before CAS_L

EECS 361


Late Read Cycle: OE_L asserted after CAS_L

Lec.16 - 21

EXAMPLE DRAM READ

(Micron MT4LC16M4A7)


READ CYCLE

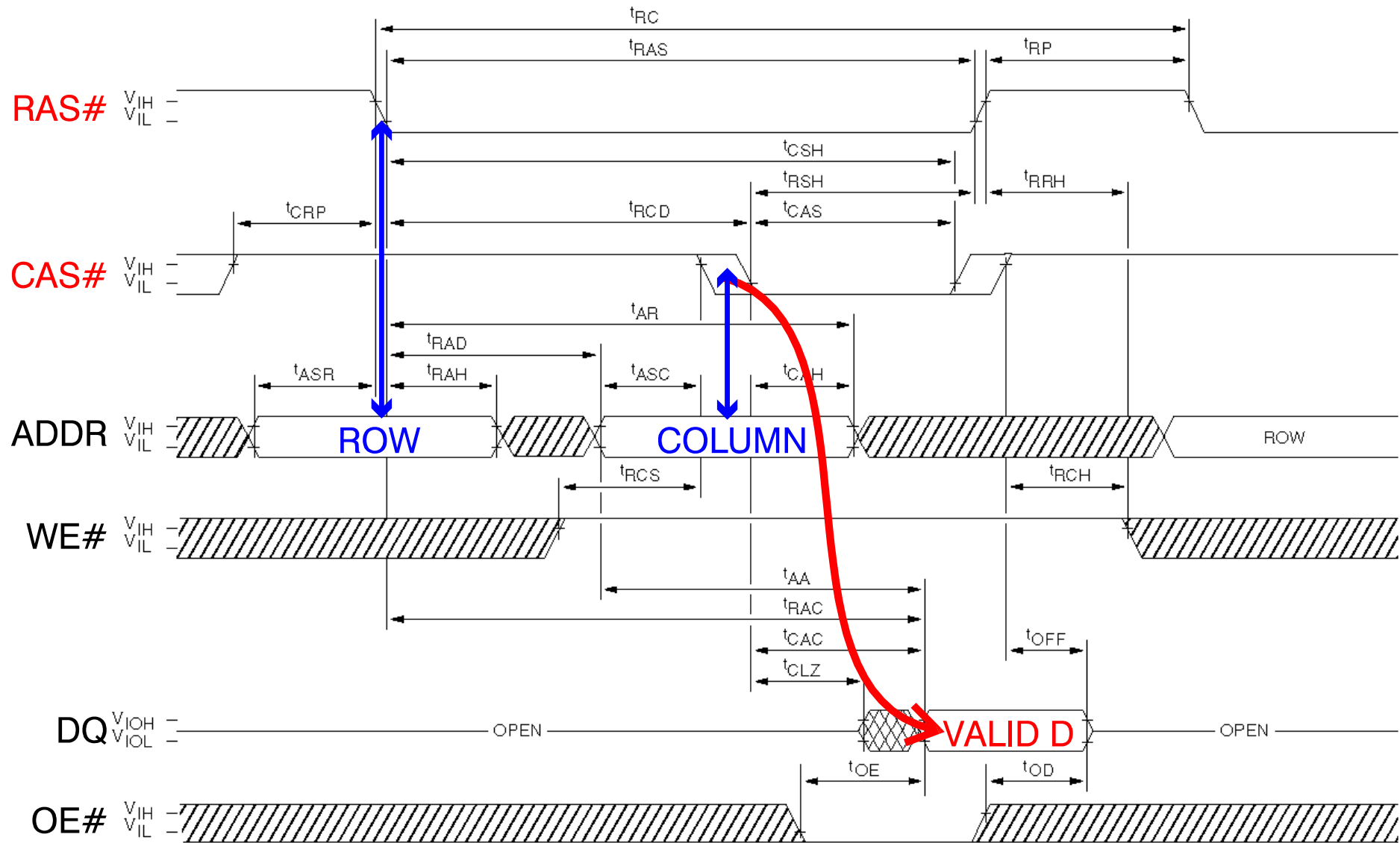

EXAMPLE DRAM WRITE

EARLY WRITE CYCLE

(Micron MT4LC16M4A7)

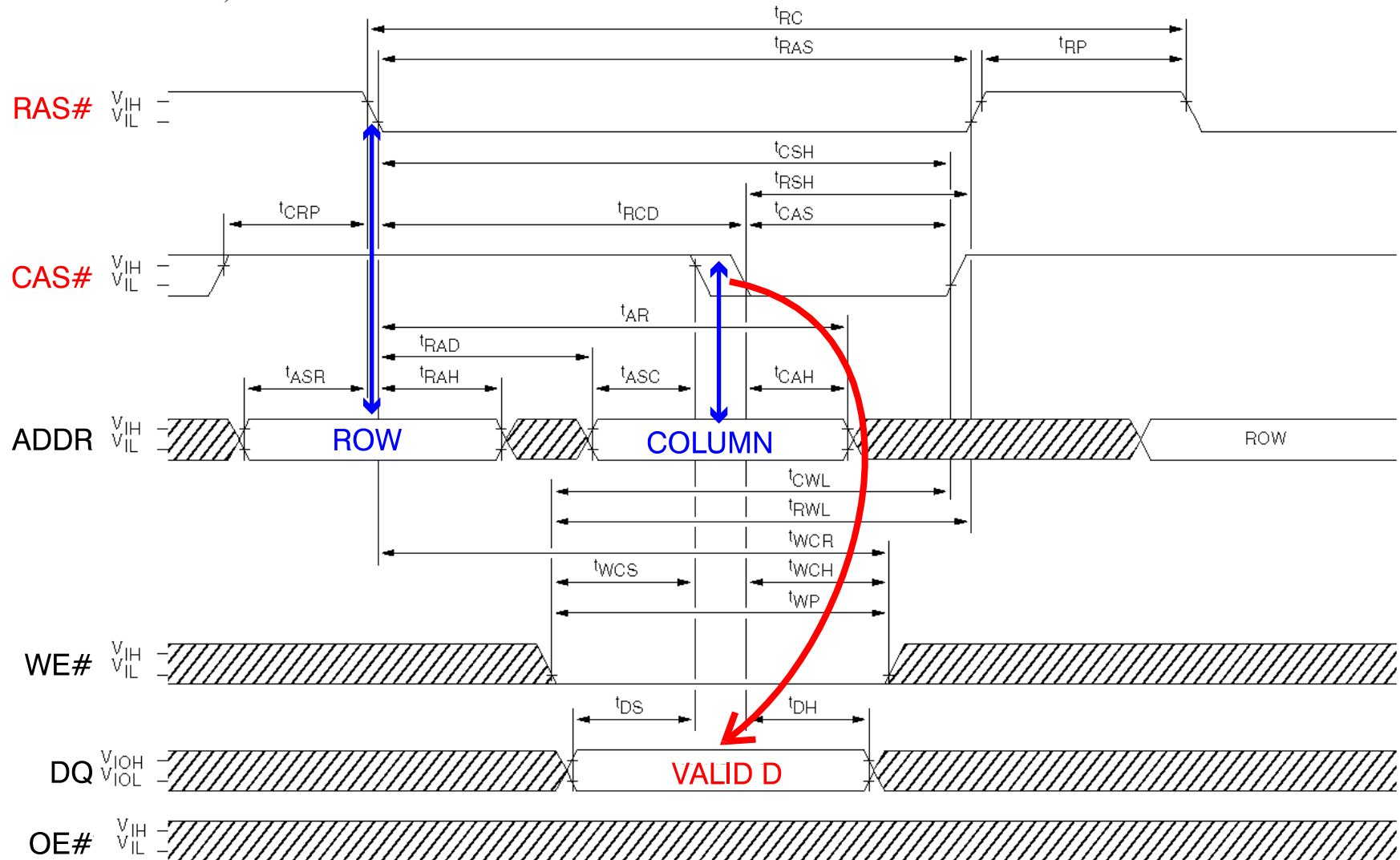

About DRAM Timing

► It's just plain ugly.


- ▷ Not at all like a nice friendly flip flop
- ▷ Lots of complex timing on control signals
- ▷ Lots of complex variations

► Why?

- ▷ DRAMs are intrinsically “Dump”
- ▷ DRAMs are intrinsically slow
- ▷ Lots of low-level tricks to disguise or mitigate this fact
- ▷ Lots of optimizations for particular hardware applications

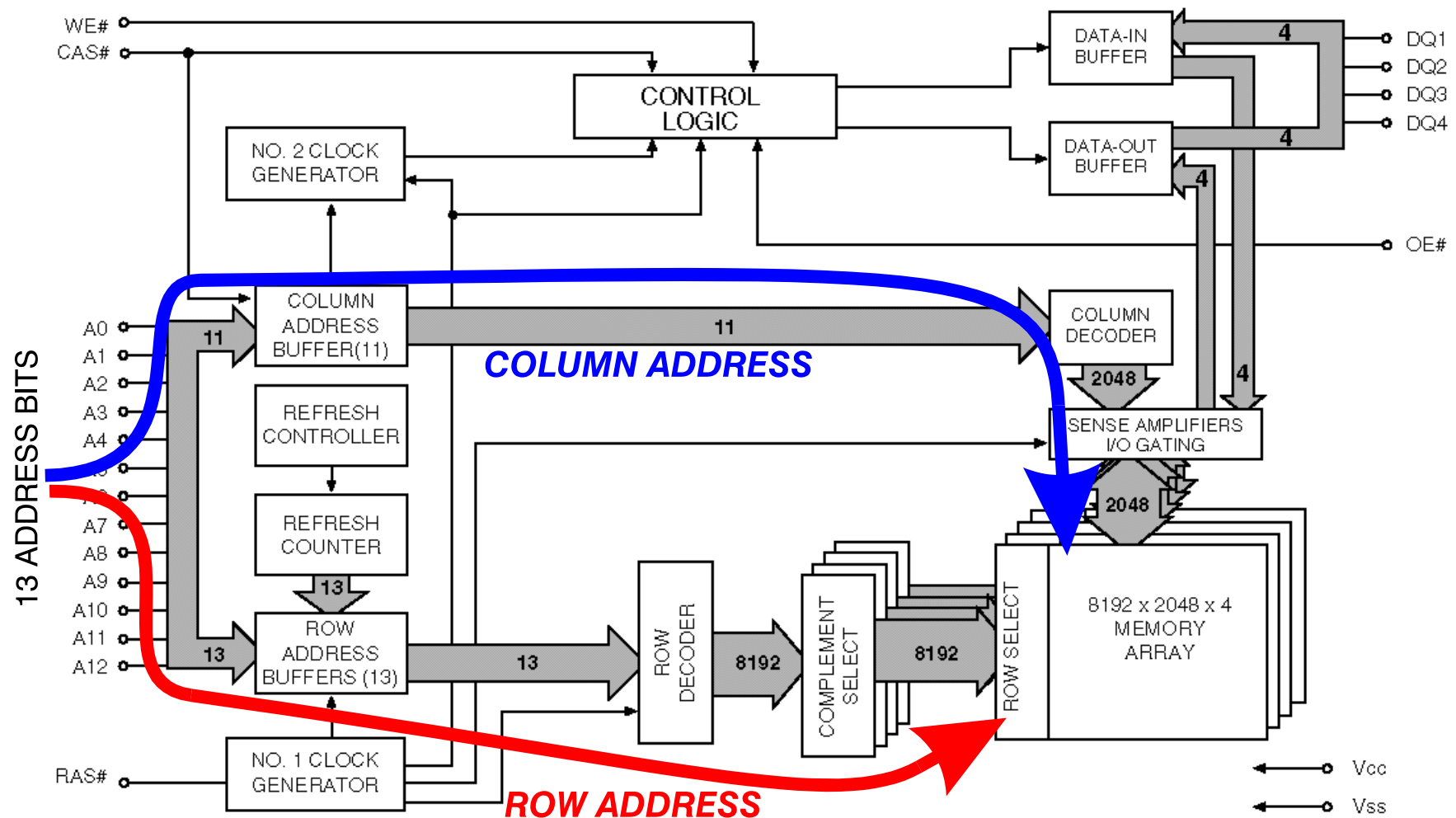Example 64Mbit DRAM: Micron

FUNCTIONAL BLOCK DIAGRAM MT4LC16M4A7 (13 row addresses)





DRAM Performance


► A 60 ns (t_{RAC}) DRAM can...

- ▷ ...perform a row access only every 110 ns (t_{RC})
- ▷ ...perform column access (t_{CAC}) in 15 ns...
- ▷ ... but time *between* successive column accesses is at least 35 ns (t_{PC}).
- ▷ (In practice, external address delays and bus wire delays make it 40 to 50 ns)

► Consequence

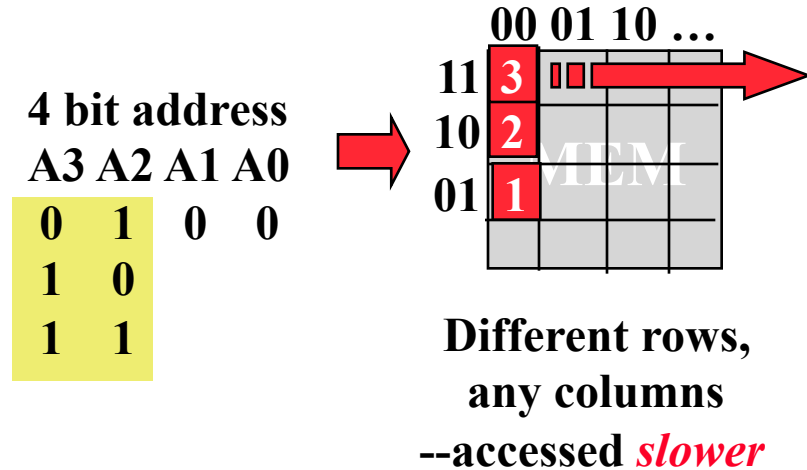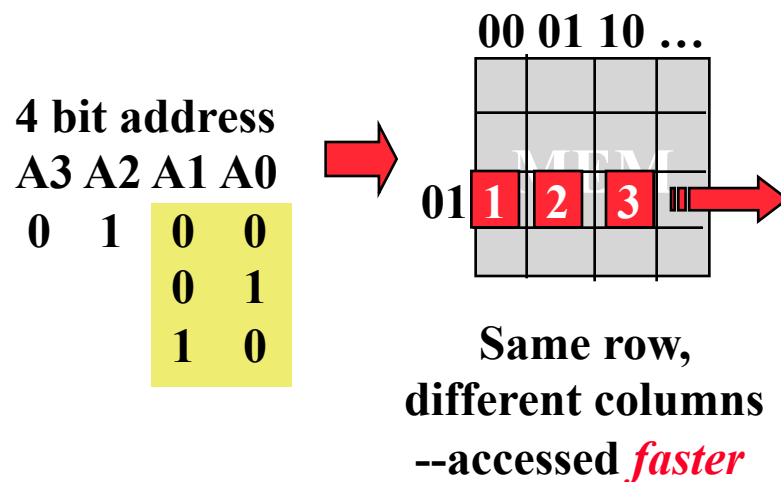


Cycle Time versus Access Time

 


- ▶ **DRAM (Read/Write) Cycle Time \gg DRAM (Read/Write) Access Time**
- ▶ **DRAM (Read/Write) Cycle Time :**
 - ▷ How frequent can you initiate an access?
 - ▷ Analogy: A little kid can only ask his father for money on Saturday
- ▶ **DRAM (Read/Write) Access Time:**
 - ▷ How quickly will you get what you want once you initiate an access?
 - ▷ Analogy: As soon as he asks, his father will give him the money
- ▶ **DRAM Bandwidth Limitation analogy:**
 - ▷ What happens if he runs out of money on Wednesday?

Increasing Bandwidth - Interleaving

Access Pattern without Interleaving:

 

Access Pattern with 4-way Interleaving:

 



Fast Page Mode DRAM

► Regular DRAM Organization:

- ▷ N rows x N column x M-bit
- ▷ Read & Write M-bit at a time
- ▷ Each M-bit access requires a RAS / CAS cycle



► Fast Page Mode DRAM

- ▷ N x M “register” to save a row

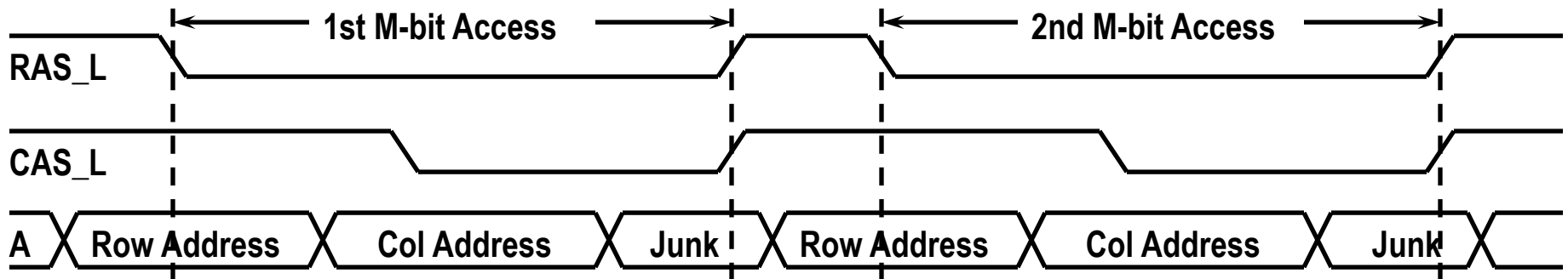 

Fast Page Mode Operation

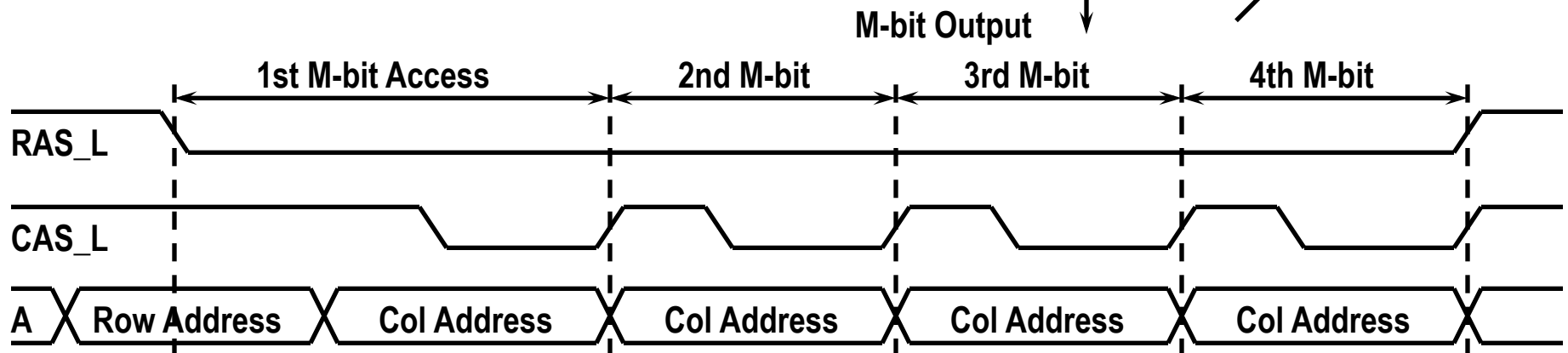 - ▶ **Fast Page Mode DRAM**
 - ▷ $N \times M$ “SRAM” to save a row
- ▶ **After a row is read into the register**
 - ▷ Only CAS is needed to access other M-bit blocks on that row
 - ▷ RAS_L remains asserted while CAS_L is toggled



DDR SDRAM Timing Diagram

- ▶ Use positive and negative edges of clock
- ▶ Request “bursts” of data
 - ▷ 4-256 words on the bus; don't re-transfer address

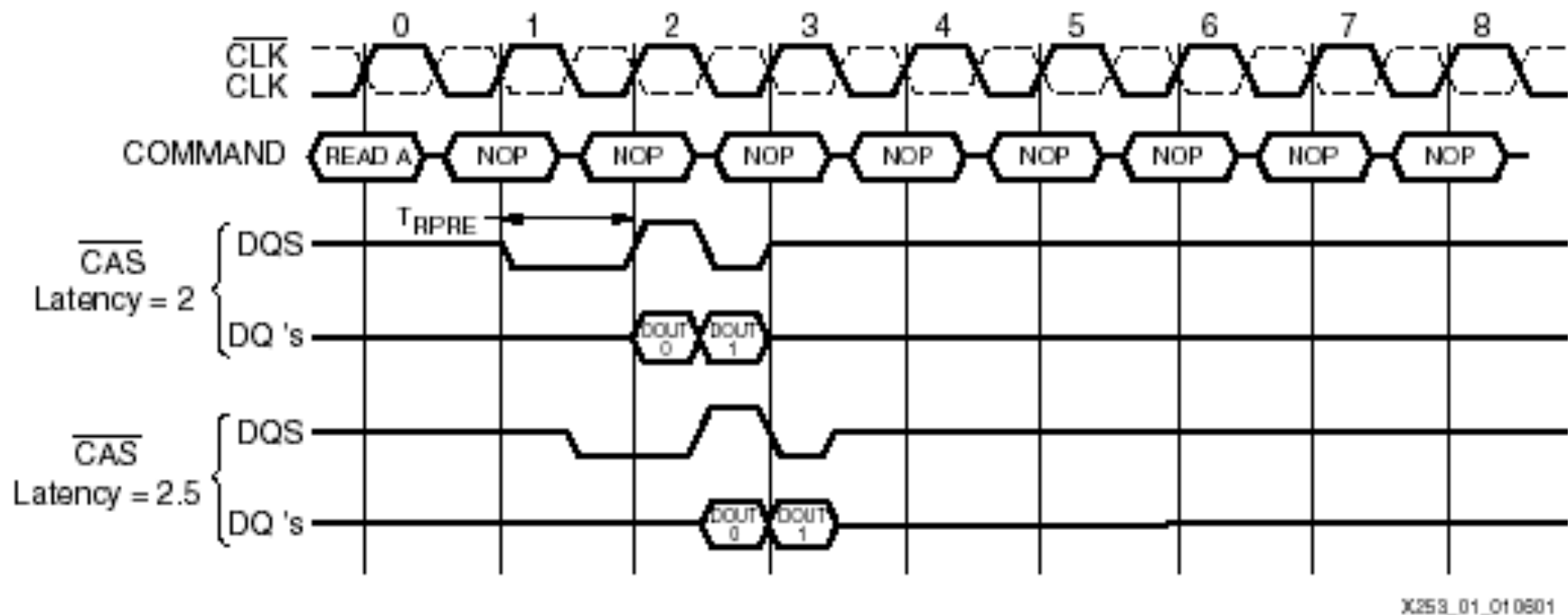



Figure 1: Burst Read Operation Timing

DRAM History

- ▶ **DRAMs: capacity +60%/yr, cost –30%/yr**
 - ▷ 2.5X cells/area, 1.5X die size in -3 years
 - ▷ DRAM fab line costs \$1B to \$2B
 - ▷ Commodity industry: high-volume, low-profit/part, conservative
- ▶ **Problems**
 - ▷ They're big and cheap, but they're still SLOW
 - ▷ SLOW is increasingly the difficult problem...


DRAM Trends

 - ▶ Exponential growth in size (bits/chip)
- ▶ Only linear improvement in speed



DRAM Bandwidth Gap

 - Means that the time to read an entire DRAM is growing slower than the size (capacity) of DRAMS; takes longer and longer to read out a whole DRAM.



DRAM: Organizational Changes

▶ **Modest organizational innovations in last 20 years**

- ▷ Example: Synchronous DRAM, Rambus DRAM
- ▷ Basically changes in how signaling occurs
- ▷ Leverage the fact that an entire row gets read every RAS cycle

▶ **More recent focus on radical signaling changes**

- ▷ Gbit signaling over essentially narrow (sometimes 1-bit serial), super-fast lines.
- ▷ Example: RAMBUS: 10X bandwidth, +30% cost
- ▷ What circuit designers worry about here (in order): (1) Cost/bit, (2) Capacity

Memory Technology Summary

▶ RAM comes in many flavors

- ▷ 2 big ones: SRAM vs DRAM
- ▷ SRAM: fast, expensive, larger silicon footprint.
- ▷ DRAM: slow, cheap, smaller silicon footprint
- ▷ Use SRAM in fast caches. Use DRAM in main memory

▶ DRAM comes in many flavors

- ▷ DRAM optimized for **capacity** more than for speed
- ▷ Secondly, DRAM is optimized for different signaling modes to speed access
- ▷ “Strange” signaling is common. Most common is need to save pins and send row-address and col-address on same wires. Leads to RAS CAS timing stuff.
- ▷ Advanced DRAM chips with sophisticated signaling are increasingly common (eg, Synch DRAM, Rambus, etc.) Goal is to break speed bottleneck in DRAM.